

Unit:

3. SINGLE PHASE AC CIRCUITS

- * Basic Elements used in AC circuits.

- 1) Resistor (R)
- 2) Inductor (L)
- 3) Capacitor (C)


- * Single Phase AC circuit

1. Purely resistive AC circuits
2. Purely inductive AC circuits
3. Purely capacitive AC circuits.

- * Purely Resistive AC Circuits :-

> Consider a simple circuit consisting of a pure resistance ' R ' ohm connected across a AC source voltage source
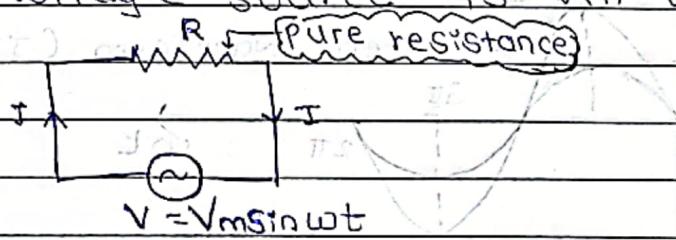
> Let AC voltage source is $V_m \sin \omega t$, ($V_m = \text{Max}$)



- * Voltage and Current Waveform

> The applied voltage is $V = V_m \sin \omega t$

> It is sinusoidal waveform having peak value = V_m

> The basic equation of current is,

$$I = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$$

$$(I \text{ in A}) : I = \left(\frac{V_m}{R}\right) \sin \omega t \text{ ampere.}$$

This equation gives instantaneous value of the current.

The standard equation of current is

$$I = I_m \sin \omega t + \phi$$

Here,



I_m = Peak (Max) value of current

ϕ = Phase difference

$$I_m = V_m \text{ and } \phi = 0$$

Thus,
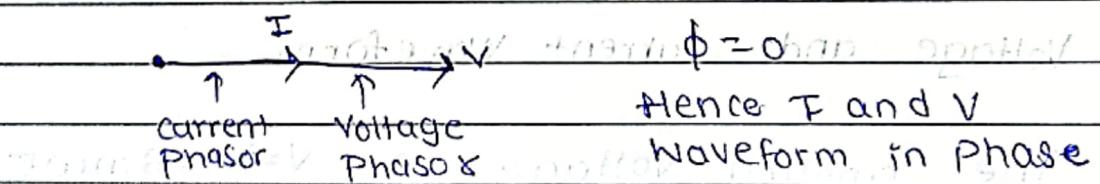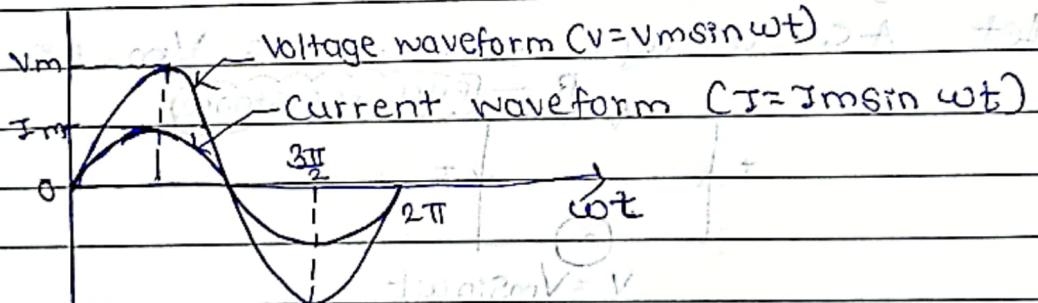
$$I = I_m \sin \omega t \text{ ampere.}$$



From the above diagram, we can say that

$$\tan \phi = \frac{V_m}{I_m} = \frac{V}{I}$$

$$9 \quad 4$$

- > The waveform of voltage and current with corresponding phasor diagram is shown in fig above.
 - > In the phasor diagram, the phasors are drawn in phase and no phase difference b/w them phasors represent the r.m.s value of the alternating quantities.
 - * Impedance of Purely Resistive circuit
 - > Impedance is the opposition provided by AC circuit to the flow of current.
 - > It is denoted by 'Z' and it is ratio of alternating voltage to the alternating current
- $\therefore Z = \frac{\text{Alternating voltage}}{\text{Alternating current}}$
- Rectangular form $Z = R + jX$ equation of impedance
 Polar form $Z = |Z| \angle \phi$

For purely resistive AC circuit, only R is present
 $X = 0$

> Impedance in rectangular form

$$Z = R + j(0)$$

$$\therefore Z = R \Omega$$

> In Polar form

$$Z = R \angle 0^\circ \Omega$$

* Expression for Power. (Purely Resistive AC circuit)

3. Instantaneous power (P)

The instantaneous power in ac circuit can be obtained by taking product of the instantaneous voltage and instantaneous current.

$$\text{Thus } P = V \cdot I$$

For purely resistive AC circuit,

$$V = V_m \sin \omega t \text{ and } I = I_m \sin \omega t$$

$$\therefore P = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$\therefore P = V_m I_m \sin^2 \omega t \quad \text{①}$$

Using trigonometric identity, $\sin^2 \omega t = \frac{1 - \cos(2\omega t)}{2}$

Equation ① becomes

$$P = V_m I_m \left[\frac{1 - \cos(2\omega t)}{2} \right]$$

$$\therefore P = \frac{V_m I_m}{2} [1 - \cos(2\omega t)]$$

$$\therefore P = \underbrace{V_m I_m}_{\text{const term}} - \underbrace{V_m I_m \cos(2\omega t)}_{\text{Fluctuating term}} \quad \dots \text{②}$$

- f) The equation of instantaneous power consist of 2 term
 First term does not contain any sine or cosine
 So it is const.

ii) Second term contains $\cos 2(\omega t)$, it will change with respect to time so it is called f..

2. Average Power (P_{av})

- > The average power of sine wave or cosine wave for one complete cycle is zero.
- > The fluctuating term is cosine wave of double frequency ($2\omega t$). So, its avg power is zero.
- > From eqⁿ ② avg power is,

$$P_{av} = V_m I_m$$


2 can be written as $2 = \sqrt{2} \cdot \sqrt{2}$

$$\therefore P_{av} = \frac{V_m I_m}{\sqrt{2} \sqrt{2}} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$\text{But } \frac{V_m}{\sqrt{2}} = V_{RMS}, \frac{I_m}{\sqrt{2}} = I_{RMS}$$

$$\therefore P_{av} = V_{RMS} I_{RMS} = N \text{ Watts.}$$

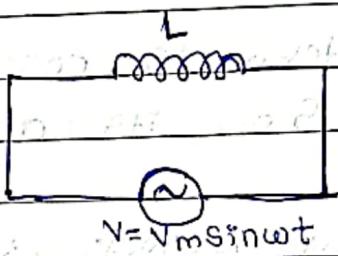- * Purely Inductive A.C. Circuit
- * Circuit Diagram
- > This circuit consists of inductor (L) connected across AC voltage source.
- > The pure inductor has zero internal resistance.
- > It is denoted by 'L' & it is measured in Henrys (H).



* Equation of current.

- > The alternating current produces alternating (changing) flux and due to this self induced emf is created.
- > This self induced emf of inductor is denoted by 'e' & given by,

$$e = -L \frac{di}{dt}$$

- > The supply voltage (V) is equal and opposite to self induced emf.

$$\therefore V = -e$$

$$= -\left(-L \frac{di}{dt}\right) = L \frac{di}{dt}$$

$$\text{Now } V = V_m \sin \omega t$$

$$\therefore V_m \sin \omega t = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_m \sin \omega t}{L}$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

Equation of current (i) can be obtain by integrating di

$$\therefore i = \int di = \int \frac{V_m}{L} \sin \omega t dt$$

$$\therefore i = \frac{V_m}{L} \int \sin \omega t dt = \frac{V_m}{\omega L} \int \cos \omega t dt$$

$$= \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$= \frac{-V_m}{\omega L} [\cos \omega t]$$

Using identity, $\cos \omega t = \sin \left(\frac{\pi}{2} - \omega t \right)$

$$\therefore i = \frac{-V_m}{\omega L} \left[\sin \left(\frac{\pi}{2} - \omega t \right) \right]$$

$$\text{But } \sin \left(\frac{\pi}{2} - \omega t \right) = \sin \left[-\left(\omega t - \frac{\pi}{2} \right) \right]$$

$$= -\sin \left(\omega t - \frac{\pi}{2} \right)$$

$$\therefore i = -\frac{V_m}{\omega L} \left[-\sin \left(\omega t - \frac{\pi}{2} \right) \right]$$

$$\therefore i = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

The term $\frac{V_m}{\omega L}$ is called as peak value, denoted by I_m

$I_m = \frac{V_m}{\omega L}$ and $\omega L = X_L = 2\pi f L$ is called as reactance of inductance.

* Voltage Current waveform:

- The voltage applied to purely inductive circuit is $V = V_m \sin \omega t$
- In case of purely inductive circuit, the current lags the voltage by an angle $\frac{\pi}{2}$ radians i.e.


The equation of current.

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

Here,

$$I_m = \frac{V_m}{X_L}$$

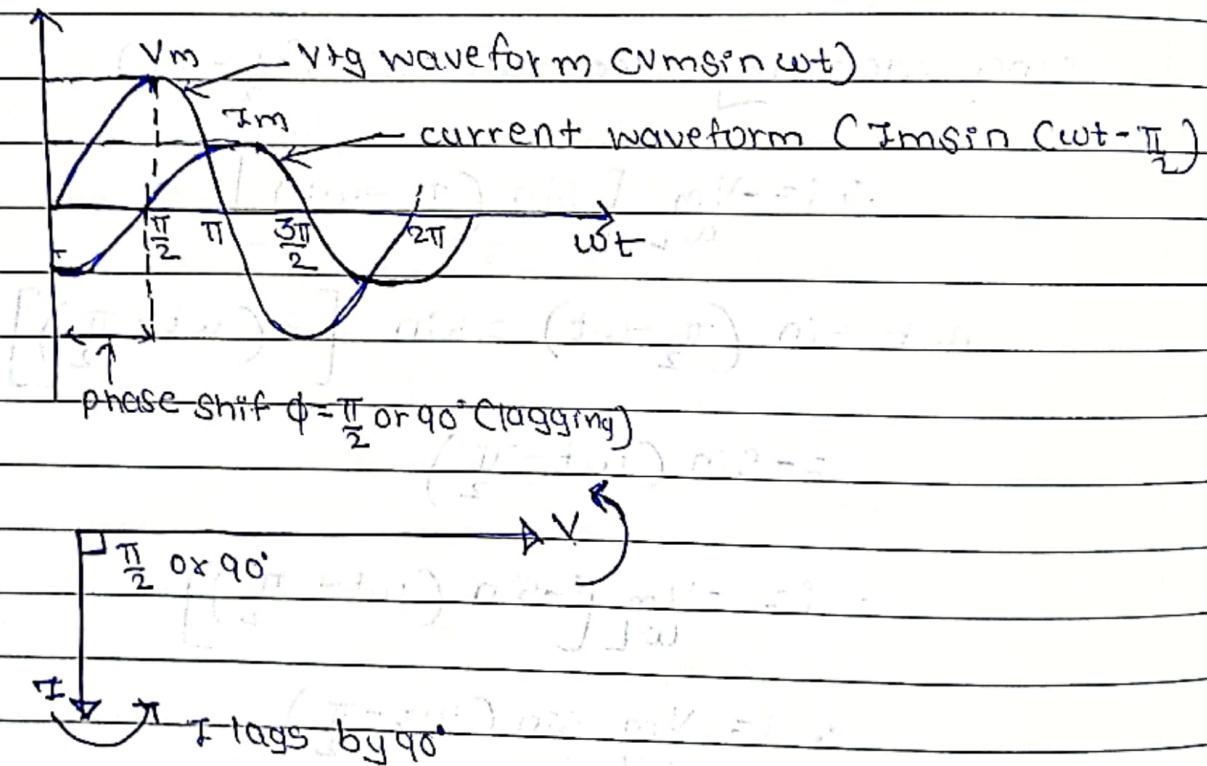X_L = Reactance of inductor
 $= \omega L = 2\pi f L$



Expression for impedance of Purely Inductive Circuit.

In rectangular form

$$Z = R + j X$$

- For purely inductive circuit, Resistance (R) is zero and reactance $= X_L$

$$\therefore Z_L = jX_L \angle 90^\circ$$

Polar form.

$$\therefore Z = X_L \angle \frac{\pi}{2} \angle 90^\circ$$

$$\text{Impedance}(Z) = \frac{V_{\text{rms}}}{\text{curr}}$$


$$= V_{\text{rms}} \angle 90^\circ - jX_L \angle 90^\circ$$

- * Inductive reactance:-
- Inductive reactance is the opposition provided by inductor to the flow of current."

> Denoted by X_L

$$X_L = \omega L \quad \text{and} \quad \omega = 2\pi f$$

$$X_L = 2\pi f L$$

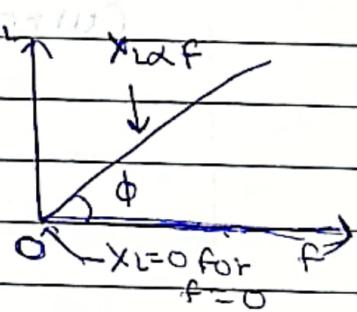


- * Purely Capacitive AC circuit

> The circuit consists of capacitor (C) connected across AC voltage source

> Capacitor has property to store electrical energy when the voltage is applied across it.
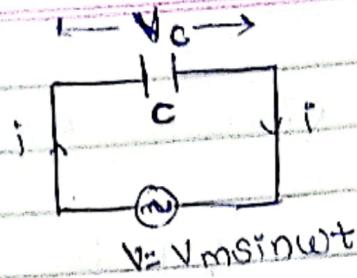
> The capacitance is denoted by 'C' and it is measured in Farads (F).



* Equation of Current:

The vtg applied to purely capacitive circuits
 $V = V_m \sin \omega t$

The current is charge the capacitor C. The instantaneous charge 'q' on the plate of capacitor is given by

$$q = CV = C V_m \sin \omega t$$

Current is the rate of change of charge

$$i = \frac{dq}{dt} = \frac{d}{dt} [CV_m \sin \omega t] = CV_m \frac{d}{dt} [\sin \omega t]$$

$$\therefore i = CV_m \omega \cos \omega t$$

$$i = V_m \cos \omega t$$

$$\frac{1}{\omega C}$$

$$\text{But } \cos \omega t = \sin (\omega t + \frac{\pi}{2})$$

$$\therefore i = \frac{V_m}{\omega C} \sin (\omega t + \frac{\pi}{2})$$

Where, $\frac{V_m}{\omega C}$ is denoted by I_m

Here ω_c is reactance of capacitance denoted by X_c

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$

* Voltage and Current Waveforms


> The voltage applied to purely capacitive circuit is

$$V = V_m \sin \omega t.$$

> For purely capacitive circuit, the current leads voltage by an angle $\frac{\pi}{2}$ radian, i.e. 90° .

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$
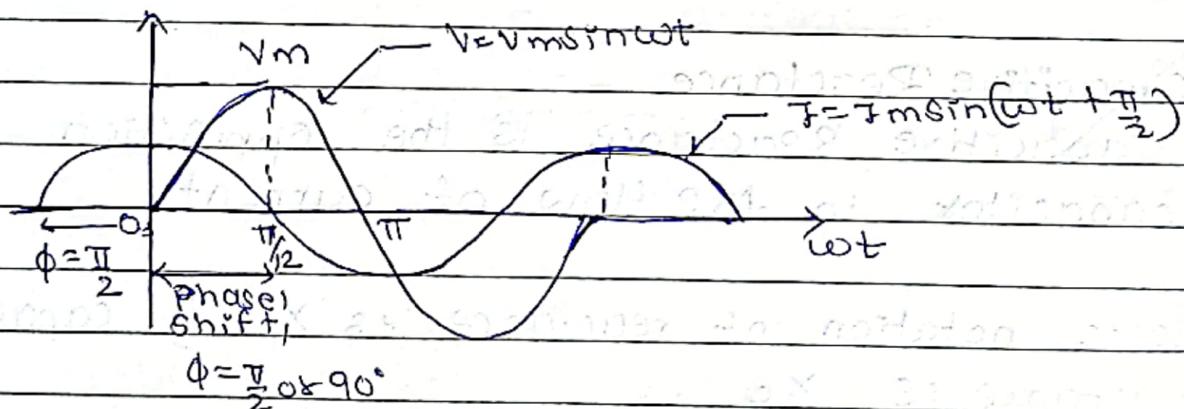
$$I_m = \frac{V_m}{X_c} \quad X_c = \frac{1}{\omega_c} = \frac{1}{2\pi f C}$$



If current leads by 90° $\Rightarrow \pi/2 \text{ or } 90^\circ$

* Impedance of Purely Capacitive Circuit
Rectangular form

$$Z = R + jX$$

- > For purely capacitive circuit, resistance (R) is zero reactance is denoted by X_C
- > Current is leading & voltage is lagging the reactance is $-X_C$

$$Z = 0 - j X_C \Omega$$

In polar form, for $-j$ term corresponding angle is $-\frac{\pi}{2}$ or 270° and 0° is angle of current.

$$\therefore Z = X_C \angle -\frac{\pi}{2} \Omega$$

$$Z = \frac{V}{I} = V \angle 0^\circ$$

$$= X_C \angle -90^\circ$$


Capacitive Reactance


- > Capacitive Reactance is the opposition provided capacitor to the flow of current.
- > Basic notation of reactance is X_C & capacitive reactance is X_C

$$X_C = \frac{1}{\omega C} \text{ and } \omega = 2\pi f$$

$$\therefore X_C = \frac{1}{2\pi f C}$$

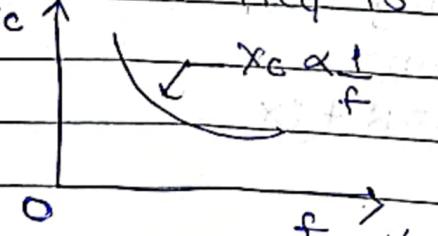- > Graph: X_C versus freq is exponential curve.



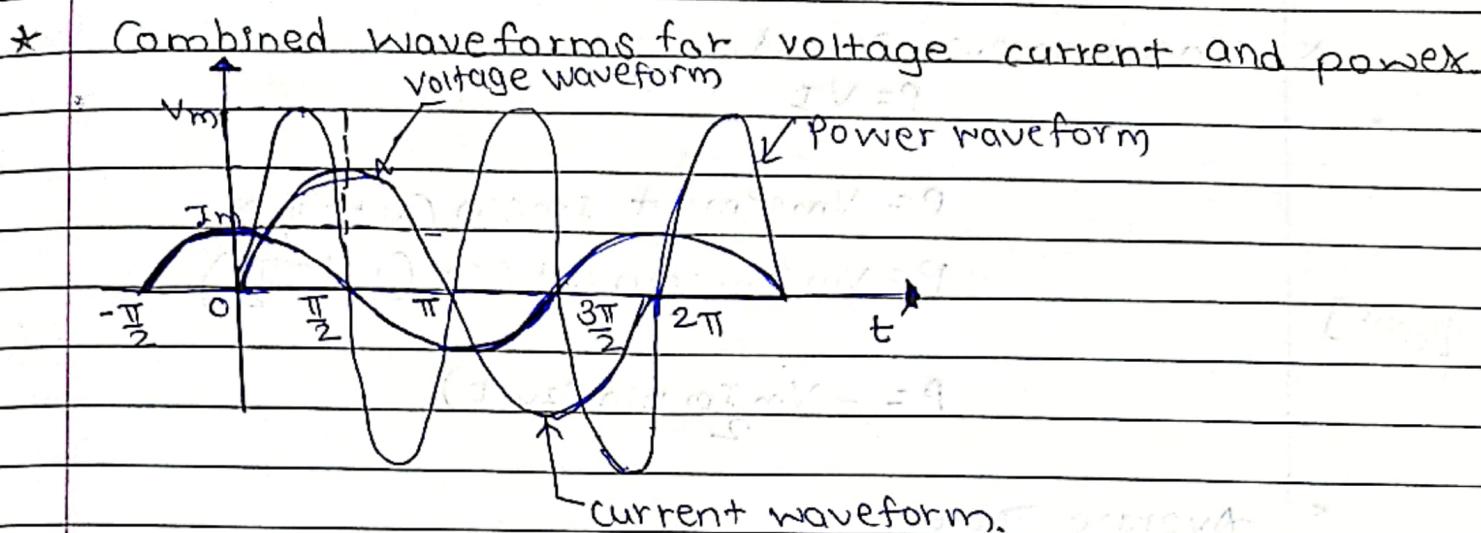

When Power is Given as, $P = V I \cos \phi$ according to $\text{Pf} = \frac{V^2}{R}$

and ϕ is angle between V and I then $P = V I \cos \phi$

or $P = V_m I_m \sin wt \cdot \sin(wt + \frac{\pi}{2}) \cos \phi$

$$\begin{aligned} P &= V_m I_m \sin wt \cdot \sin(wt + \frac{\pi}{2}) \cos \phi \\ &= V_m I_m \sin wt \cdot \sin(wt + \frac{\pi}{2}) \cos \frac{\pi}{2} \end{aligned}$$

$$P_{\text{avg}} = 0$$


- * In case of capacitor average power (P_{avg}) for a complete cycle is always zero but the energy stored by capacitor

$$E = \frac{1}{2} C V^2 \text{ Joules}$$

Because $E = \frac{1}{2} C V^2$ stored energy becomes zero

(Ex) $Q = Q_0 \sin \omega t$ $V = V_0 \sin \omega t$

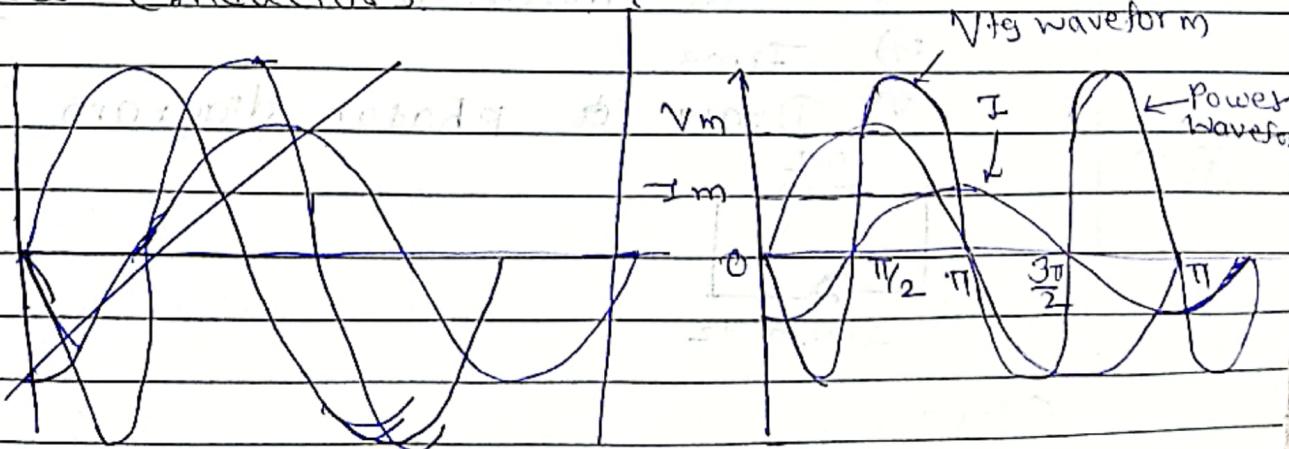- * Combined waveform for voltage current & power (Inductor)



* Instantaneous power.

$$P = VI$$

$$P = V_m s \sin \omega t I_m \sin (\omega t - \frac{\pi}{2})$$

$$P = V_m I_m \sin \omega t \sin (\omega t - \frac{\pi}{2})$$

$$P = -\frac{V_m I_m}{2} \sin (2\omega t)$$

* Average Power

The average power in case of an inductor complete cycle is always 0, because \oplus and \ominus half cycle of power waveform cancel each other but the energy stored is always

$$E = \frac{1}{2} L I^2 \text{ and } E = \frac{1}{2} C V^2$$

$$P_{av} = 0$$

Q) Numerical:-

Q] An inductive coil having 0.1 Henry Inductance is connected across 200V, 50Hz supply find i) inductive reactance (X_L)


ii) RMS value of current (I_{rms})

iii) V_{max} maximum value of V_{tg}

iv) I_{rms} .

v) Draw a phasor diagram.

Given

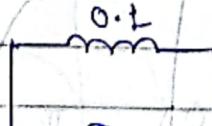

200V, 50Hz

Given,

$$L = 0.1 \text{ H}$$

$$V_{rms} = 200 \text{ V}$$

$$; f = 50 \text{ Hz}$$

i) Inductive reactance (X_L)

$$X_L = 2\pi f L$$

$$= 2 \times 3.14 \times 2 \times \pi \times 50 \times 0.1$$

$$= 314.159 \Omega$$

ii) $V_{rms} = \frac{V_m}{\sqrt{2}}$

$$200 = \frac{V_m}{\sqrt{2}}$$

$$200\sqrt{2} = V_m$$

$$\boxed{V_m = 282.84 V}$$

iii) $I_m = \frac{V_m}{X_L}$

$$I_m = 282.84$$

$$314.1$$


$$\boxed{I_m = 0.89 A}$$

iv) $I_{rms} = \frac{I_m}{\sqrt{2}}$

$$= \frac{0.89}{\sqrt{2}}$$

$$I_{rms} = 0.63 A$$

v)

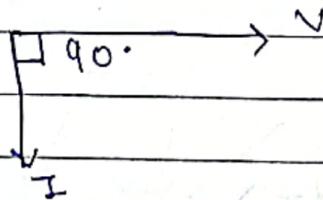

$$V = V_m \sin \omega t \quad \left\{ \begin{array}{l} i = I_m \sin (\omega t - \frac{\pi}{2}) \end{array} \right.$$

$$= 282.84 \sin 2\pi \times 50 t \quad \left\{ \begin{array}{l} i = 0.89 \sin (2\pi \times 50 t - \frac{\pi}{2}) \end{array} \right.$$

$$V = 282.84 \sin 100\pi t \quad \left\{ \begin{array}{l} i = 0.89 \sin (100\pi t - \frac{\pi}{2}) \end{array} \right.$$

equation
of voltage

$\left\{ \begin{array}{l} \text{eqn of current} \\ \text{v} \end{array} \right.$

(Q2) Find the expression for current if will flow through pure inductor 0.2 H connected across 230 V 50 Hz AC supply. Draw the phasor diagram.

Ques

Given;

$$L = 0.2\text{ H}$$

$$V_{rms} = 230\text{ V}$$

$$f = 50\text{ Hz}$$

$$X_L = 2\pi f L$$

$$= 2 \times \pi \times 50 \times 0.2$$

$$X_L = 62.83$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$230 \times \sqrt{2} = V_m$$

$$V_m = 325.269\text{ V}$$


$$I_m = \frac{V_m}{X_L}$$

$$I_m = \frac{325.269}{62.83}$$

$$\boxed{I_m = 5.176}$$

$$I = I_m \sin(\omega t - \frac{\pi}{2})$$
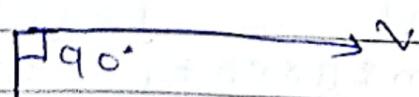
$$I = 5.176 \sin(100\pi t - \frac{\pi}{2})$$



$$I = 5.176 \sin(100\pi t - \frac{\pi}{2})$$

Capa

Q.3) 50 μF capacitor is connected across 230V, 50 Hz supply calculate

- 1) Capacitive reactance (X_C) or reactance offered
- 2) Max value of current
- 3) Max value of V_{tg}
- 4) Write eq'n of V_{tg} and current
- 5) Phasor diagram.


(PQn)

Given,

$$C = 50 \mu F = 50 \times 10^{-6} F$$

$$V_{rms} = 230 V$$

$$F = 50 \text{ Hz}$$

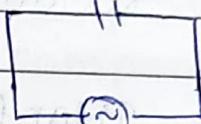

$$\therefore X_C = \frac{1}{2\pi F C} = \frac{1}{2\pi \times 50 \times 10^{-6} \times 50} \\ X_C = 53.661 \Omega$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$230\sqrt{2} = V_m$$

$$[V_m = 328.269]$$


$$\therefore I_m = \frac{V_m}{X_C} = \frac{328.269}{53.661} \\ I_m = 5.109 A$$

$$\therefore I = I_m \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$I = 5.109 \sin \left(100\pi t + \frac{\pi}{2} \right)$$

$$V = 328.269 \sin(100\pi t)$$

Phasor Diagram: -

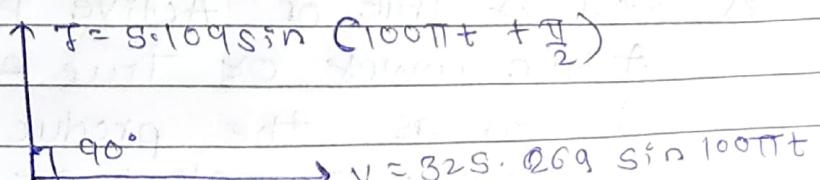

Impedance:-

The opposition provided by AC circuit to the flow of current is called as impedance.

3 basic elements of AC circuit

Resistor ii) Inductor iii) Capacitor

Denoted by Z


Rectangular form:-

$$Z = R + jX$$

Polar form:-

$$Z = |Z| \angle \phi$$

Impedance Triangle:-

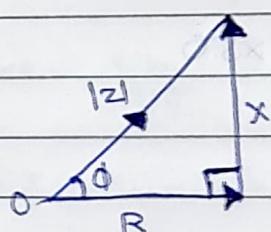

Types of Power

Apparent Power (S)

"Apparent power is defined as the product of RMS value of voltage and RMS value of current."

Denoted by ' S '

Unit:- Volt-Ampere (VA)

Formula;

$$S = V_{\text{rms}} \times I_{\text{rms}}$$

Real or True or Active Power (P)

Active power or True P or Real P is

defined as the product of Supply voltage and active component of current (I_{rms})

- > Denoted by 'P'
- > Unit : Watt (W)

Formula: $P = VI \cos \phi$,
 rms current
 rms voltage phase betw' v & I

3) Imaginary or Reactive Power (Q)

Reactive Power is defined as the product of supply voltage and reactive component of current ($I \sin \phi$)

- > Denoted by 'Q'
- > Unit :- Volt - Ampere Reactive (VAR).

Formula: $Q = VI \sin \phi$,

* Power Factor ($\cos \phi$)

It is defined as ratio of real power (P) to apparent power (S),

$$P = VI \cos \phi \quad S = VI$$

$$P.F = \frac{VI \cos \phi}{VI} = \cos \phi$$


- > Ratio of Resistance (R) to the impedance (Z)

$$P.F = \cos \phi = \frac{R}{Z}$$

$P.F = \cos \phi = \frac{\text{Fundamental Component of current}}{\text{RMS value of total current}}$

- * Significance (Imp) of Power factor
 - i) Ideally PF must be equal to 1.
 - ii) High P.F increases current carrying capacity.
 - iii) For improved P.F, power losses are reduced.

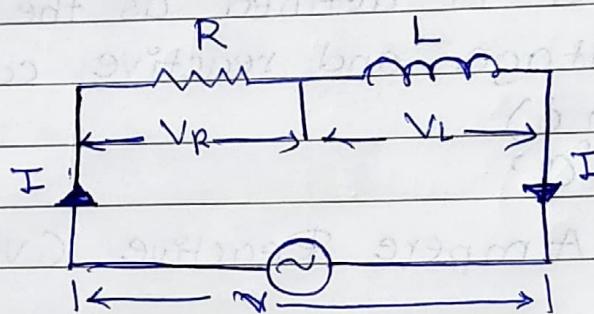* A.C through Series combination of R-L circuit



Consider a simple circuit consisting of series combination of Resistance (R) and inductance (L) connected across V.

The supply voltage is, $V = V_{ms} \sin \omega t$

Let $V = V_{rs}$ be equal to rms value of applied voltage
 rms value of resultant current Hence
 voltage drop across R


$$V_R = I \times R \quad (V_R \text{ in phase with current})$$

Voltage drop across L

$$V_L = I \times X_L \quad (V_L \text{ leading the current by magnitude})$$

* Phasor Diagram

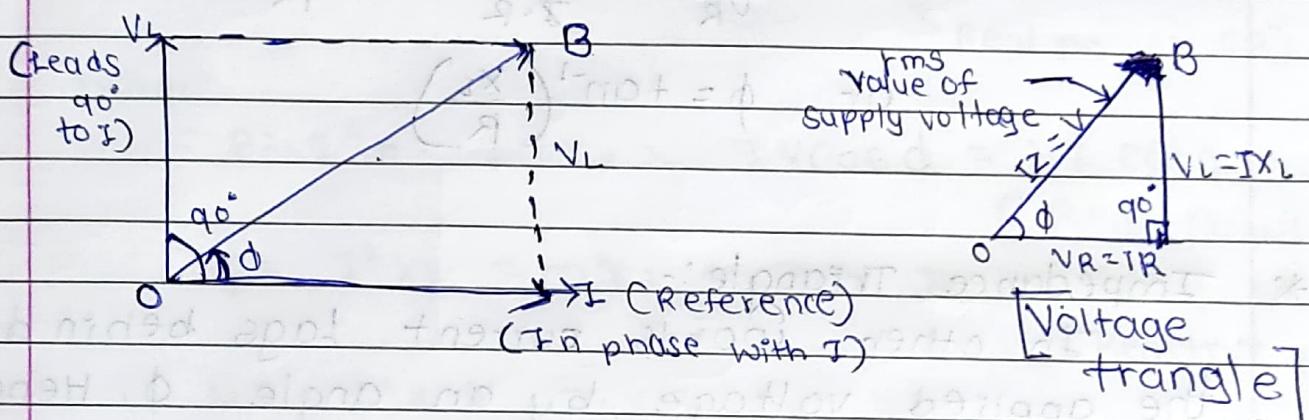As resistance R and inductance L are in Series, their individual voltage drops V_R and V_L also come in series. Therefore total voltage is found by phasor addition. Current is taken as reference in series circuit as it is common in both the elements if it is drawn on positive x-axis as shown.



* Impedance of Series AC R-L

From vtg triangle, OB represents total applied voltage which is vector sum of V_R and V_L .

$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\text{But } V_R = IR$$

$$V_R^2 = I^2 R^2$$

$$V_L = IX_L$$

$$V_L^2 = I^2 X_L^2$$

$$V = \sqrt{I^2 R^2 + I^2 X_L^2}$$

$$= \sqrt{I^2 (R^2 + X_L^2)}$$

$$V = I \sqrt{R^2 + X_L^2}$$

$$Z = \frac{V}{I} \quad \text{i.e. } V = IZ$$

$$\therefore Z = \sqrt{R^2 + X_L^2}$$

- > Z is known as impedance of the circuit
- > As shown in phasor diagram applied voltage leads the current I by an angle ϕ such that



$$\tan \phi = \frac{V_L}{V_R} = \frac{\pi \cdot X_L}{\pi \cdot R} = \frac{X_L}{R}$$

$$\text{or } \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

* Impedance Triangle:-

In other words current lags behind the applied voltage by an angle ϕ , Hence

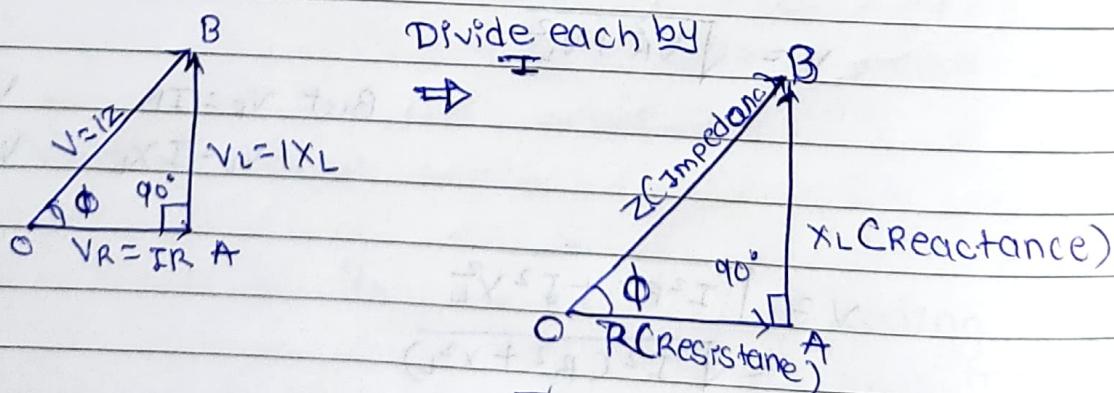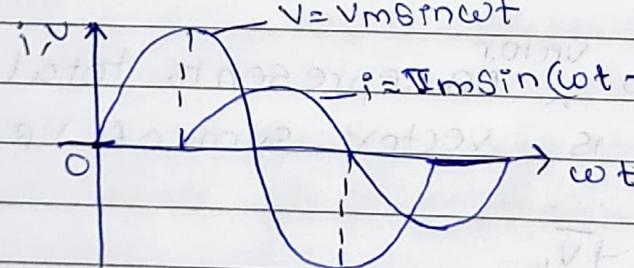
$$V = V_m \sin \omega t \quad \text{and current } i = I_m \sin(\omega t - \phi).$$



[Impedance Triangle]

* Power triangle

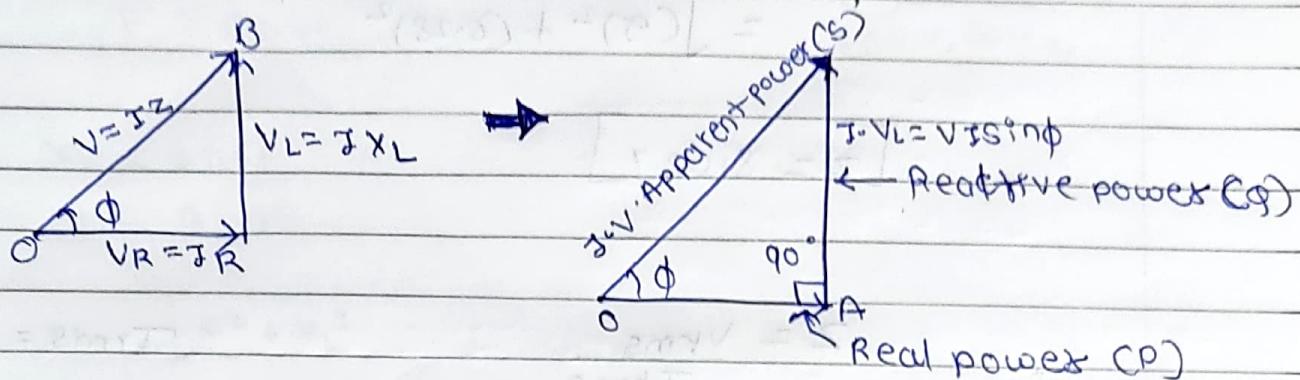Power triangle is obtained by multiplying each side of voltage triangle by current (I)



Where,

$$P = I^2 R = I \cdot V R_R = I \cdot V \cos \phi = V I \cos \phi \text{ watt}$$

(Real power)

$$Q = I^2 X_L = I \cdot V_L = I \cdot V \sin \phi \text{ VAR}$$

(Reactive power)

$$S = I^2 Z = I \cdot V = V I \text{ VA}$$

(Apparent power)

- Q) A coil has inductance 20 mH and resistance of 5 Ω connected in series across the voltage of $V = 48 \sin(314t)$ obtain the expression for current drawn by.

Given,

$$L = 20 \text{ mH} = 20 \times 10^{-3} \text{ H}$$

$$R = 5 \Omega$$

$$V = V_m \sin \omega t$$

$$V = 48 \sin(314t)$$

$$\boxed{V_m = 48}$$

$$X_L = 2\pi f L$$

$$= 2\pi \times 49.97 \times 20 \times 10^{-3}$$

$$X_L = 6.28$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(5)^2 + (6.28)^2}$$

$$[Z = 8.027]$$

$$Z = \frac{V_{rms}}{I_{rms}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$= \frac{48}{8.027}$$

$$\cos \phi = \frac{R}{Z}$$

$$\phi = \cos^{-1} \left(\frac{R}{Z} \right)$$

$$\phi = 51.47^\circ$$

$$I = I_m \sin(\omega t - \phi)$$

$$= 31.4 \sin(314t - 51.47^\circ) \text{ A}$$

$$= 31.4 \sin(314t - 51.47^\circ) \text{ A}$$

- g) A series R-L circuit $R = 25 \Omega$ and $L = 0.1 H$ are connected in series across $250 V, 50 Hz$ supply. Calculate:

- 1) Inductive Reactance (X_L)
- 2) Impedance (Z)
- 3) Current (I)
- 4) Power factor
- 5) Real, Reactive, Apparent power
- 6) Draw the phasor diagram


Q101ⁿ Given,

$$R = 25 \Omega$$

$$L = 0.1 \text{ H}$$

$$V_{\text{rms}} = 250 \text{ V}$$

$$F = 50 \text{ Hz}$$

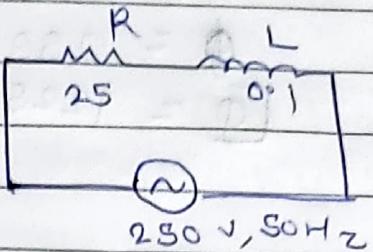

i)

$$X_L = 2\pi f L$$

$$X_L = 31.45$$

ii)

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(25)^2 + (31.45)^2}$$

$$Z = 40.148$$

iii)

$$\mathbf{V} = I Z$$

$$I = \frac{\mathbf{V}}{Z} = \frac{250}{40.148}$$

$$I = 6.266 \text{ A}$$

iv)

$$P = V I \cos \phi$$

$$\phi = \cos^{-1}(R/Z)$$

$$= \cos^{-1}\left(\frac{25}{40.148}\right)$$

$$P = V I \cos(51.48)$$

$$P = 250 \times 6.266 \cos(51.48)$$


$$P = 975.97 \text{ watt}$$

$$\begin{aligned} \phi &= VI \sin \phi \\ \phi &= 250 \times 6.266 \times \sin(51.48) \\ \phi &= 1225.615 \text{ VAR} \end{aligned}$$

$$S = VI$$

$$\begin{aligned} &= 250 \times 6.266 \\ [S] &= 1566.5 \text{ VA} \end{aligned}$$

* A-C through series R-C circuit.

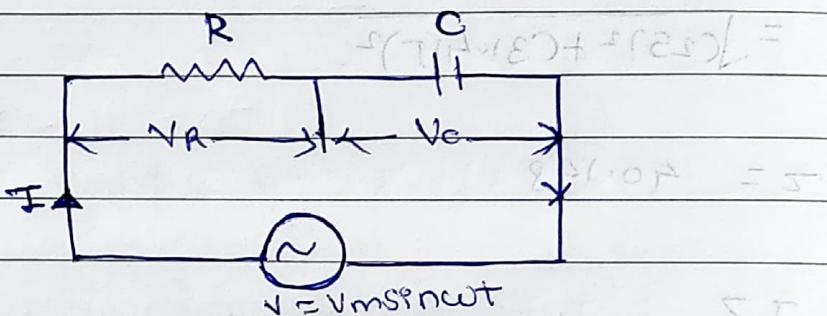

Consider series combination of resistance and capacitance connected across voltage (V)

The ^{Supply} voltage drop across is $V = V_m \sin \omega t$

If instantaneous current 'i' then RMS current is denoted by I_{rms} or I .

Due to flow of current 'i', the voltage drop take place across resistor (R) and capacitor (C)

The voltage drop across Resistance $R = V_R$

$V_R = I \times R$... ① (V_R in phase with I)

V_R & I are in phase (I)

Cuto across resistor

The voltage drop across capacitance $C = V_c$

$$V_c = I \times X_C$$

$$X_C = \frac{1}{2\pi f C}$$


↓
capacitive
Reactance

V_c lags the I by 90°


As V_R and V_c are voltage drop across R and C therefore total voltage V is phasor sum of V_R and V_c

$$V = V_R + V_c$$

* Complete phasor diagram.

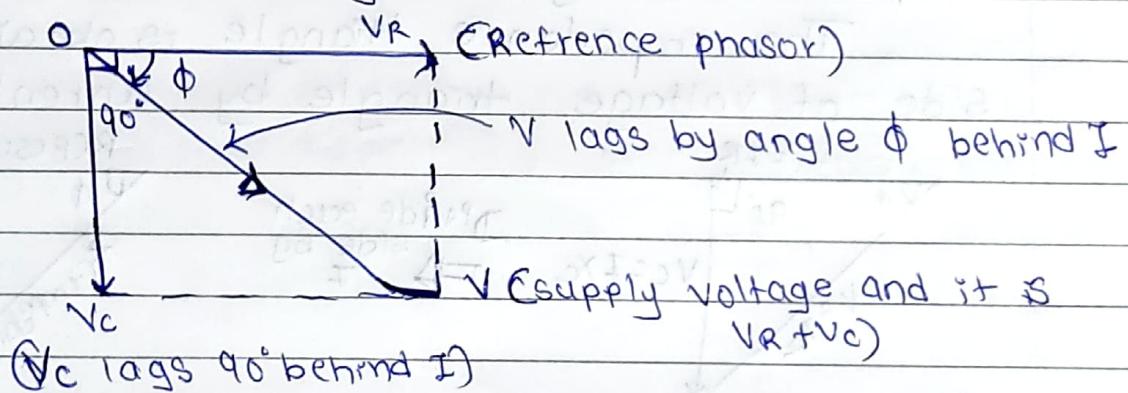

* Voltage triangle:

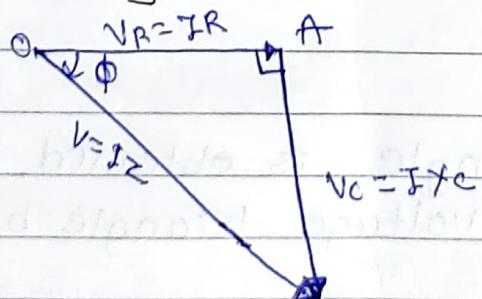

• Impedance

From vtg triangle.

$$V = \sqrt{V_R^2 + V_C^2}$$

$$\text{But } V_R = IR \quad \therefore V_R^2 = I^2 R^2$$

$$V_C = IX_C \quad \therefore V_C^2 = I^2 X_C^2$$

$$V = \sqrt{I^2 R^2 + I^2 X_C^2} = \sqrt{I^2 (R^2 + X_C^2)}$$

$$V = I \sqrt{R^2 + X_C^2}$$

$$Z = \frac{V}{I}$$


$$V = ZI$$

$$\therefore Z = \sqrt{R^2 + X_C^2}$$

$$V + jV = V$$


* Impedance triangle

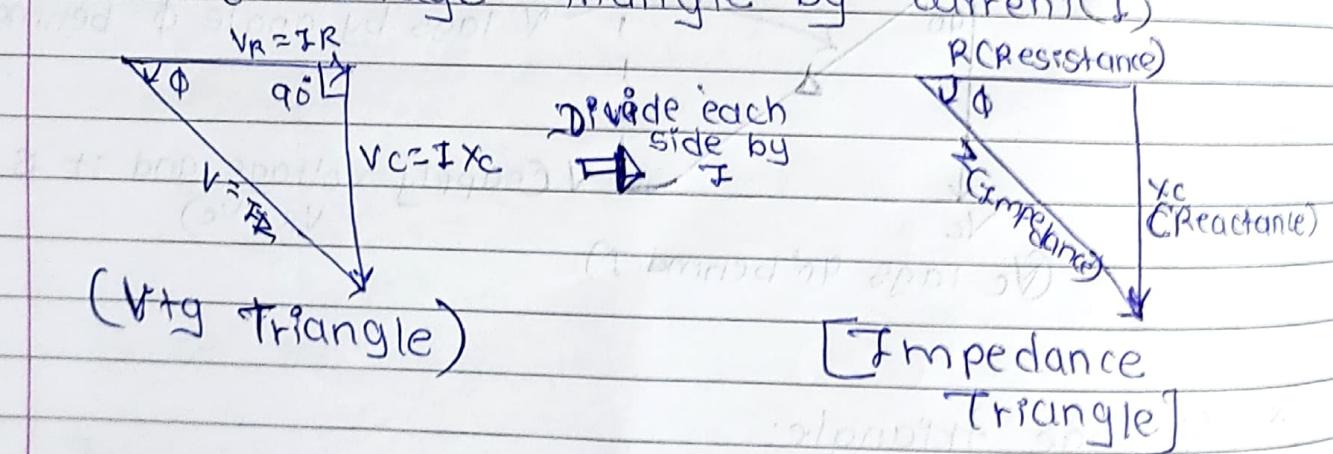The impedance triangle is obtained by dividing side of voltage triangle by current (I)




* Power Triangle:

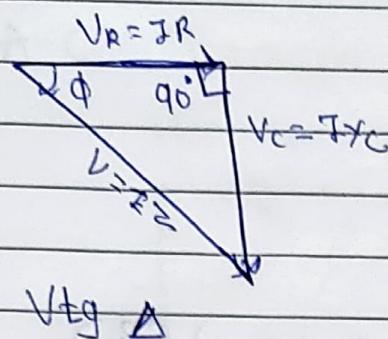Power Triangle is obtained by multiplying each side of voltage triangle by current (I)



multiply
each side
by I

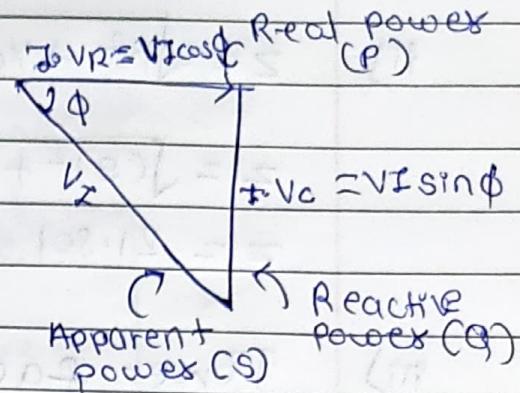

[Power Triangle]

$$\tan \phi = -\frac{V_C}{V_R}$$

$$\phi = \tan^{-1} \left(-\frac{V_C}{V_R} \right)$$

$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X^2}}$$

$$\phi = \cos^{-1} \left(\frac{R}{Z} \right)$$

(Q) A series circuit consisting of Resistance 5Ω and capacitance of $150\mu F$ is connected to single phase $200V$, $50Hz$ supply. Calculate.

- i) Capacitive Reactance
- ii) Impedance
- iii) Power factor.
- iv) Current drawn by circuit
- v) Actual Power or Real power.

Ques Given,

$$i) X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times \pi \times 50 \times 150 \times 10^{-6}}$$

$$[X_C = 21.22 \Omega]$$

ii) $Z = \sqrt{R^2 + X_C^2}$

$$Z = \sqrt{(5)^2 + (21 \cdot 220)^2}$$

$$Z = 21.80$$

iii) Power factor $= \cos \phi \Rightarrow \phi = \cos^{-1} \left(\frac{R}{Z} \right)$
 $P.F = 0.229 \quad \phi = 76.74^\circ$

iv) $V = I \times Z$

$$I = \frac{V}{Z}$$

$$I = \frac{200}{21.80}$$


$$I = 9.173$$

v) $P = V I \cos \phi$

$$= 200 \times 9.173 \cos (76.74^\circ)$$

$$P = 420.771$$

* A-C Through R-L-C circuit.

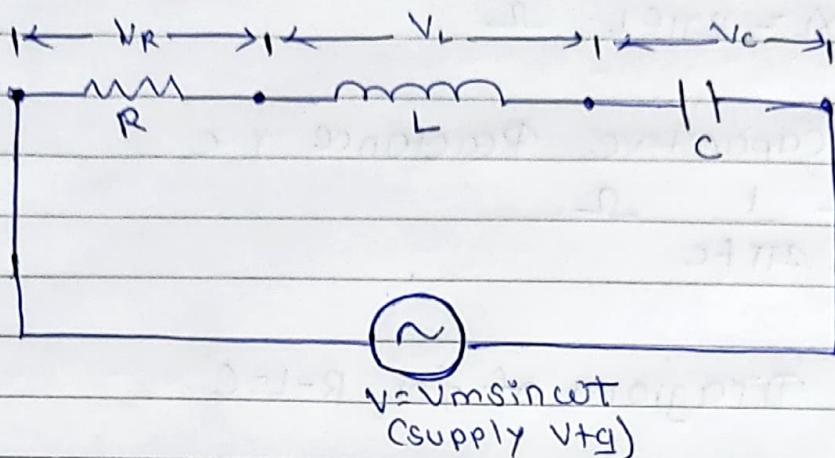


The supply voltage is $V = V_m \sin \omega t$

Consider a series combination of resistor (R), inductor (L) & capacitor (C) connected across a voltage (V)

Due to flow of current I, the voltage drop take place across R, L, C.


Voltage drop across Resistance R
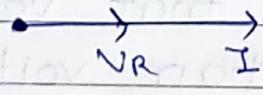
$$V = IR \quad (V_R \text{ in phase with } I)$$



Voltage drop across Inductor L


$$V_L = IXL$$

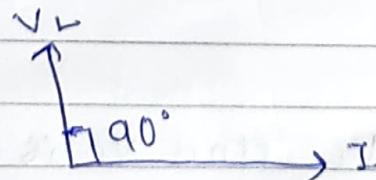

(V_L leads the current I by 90°)

Voltage drop across capacitor C

$$V_C = IXC$$

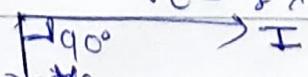

(V_C lags the I by 90°)

X_L = Inductive Reactance

$$\text{i.e. } X_L = 2\pi f L \quad \Omega$$

X_C = Capacitive Reactance i.e.

$$X_C = \frac{1}{2\pi f C} \quad \Omega$$

* Phasor Diagram of R-L-C


Q Explain the series R-L-C circuit with three cases

i) $X_L > X_C$

ii) $X_L < X_C$

iii) $X_L = X_C$

i) Phasor Diagram for $X_L > X_C$


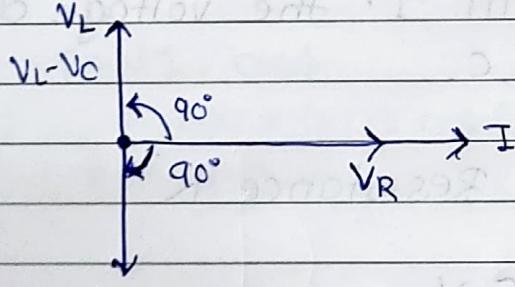


As $X_L > X_C$ it means that voltage drop across L is greater than voltage drop across C

$$\therefore V_L > V_C$$


Thus the resultant of V_L and V_C will be towards V_L

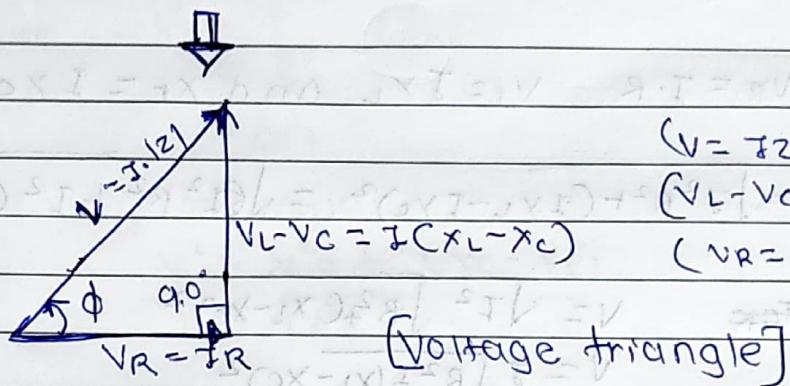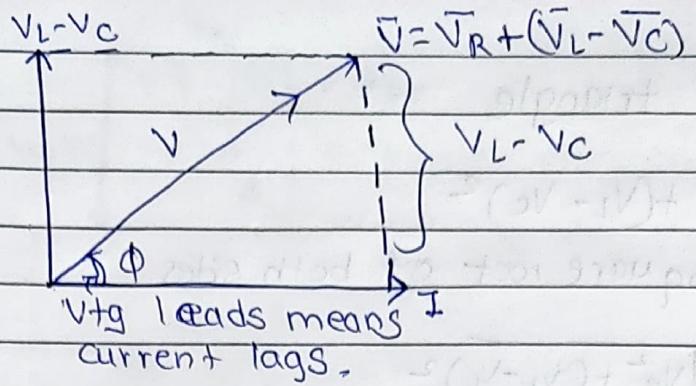The resultant of V_L and V_C is $V_L - V_C$




- * Impedance triangle is obtained by dividing each side of V_{tg} triangle by current I .

\Downarrow Divide each side by I

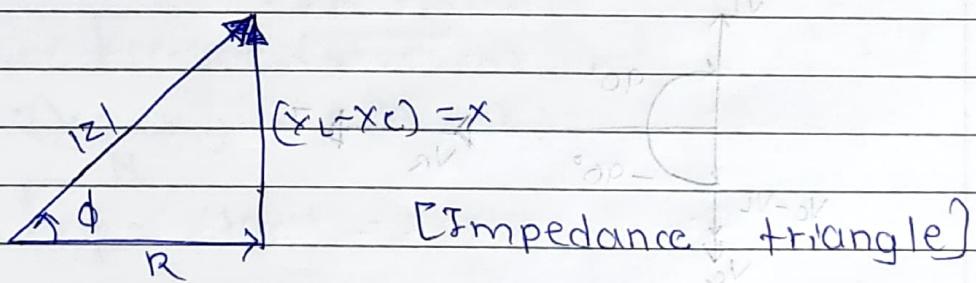

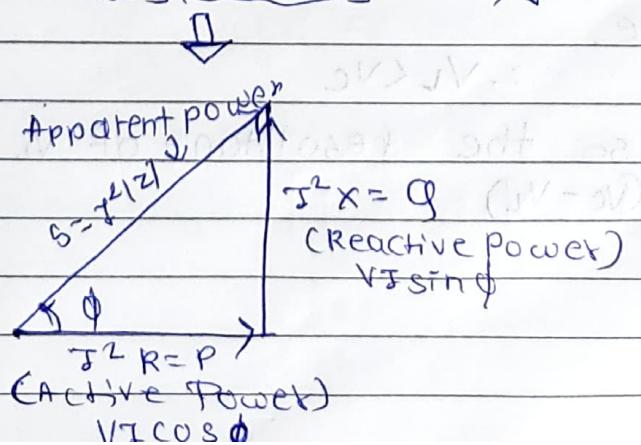- * Power triangle is obtained by multiplying each side of V_{tg} triangle by I^2 .



from vtg triangle

$$V^2 = V_R^2 + (V_L - V_C)^2$$

Taking square root of both sides

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

Now $V_R = I \cdot R$, $V_L = I X_L$ and $X_C = I X_C$


$$V = \sqrt{I^2 R^2 + (I X_L - I X_C)^2} = \sqrt{I^2 R^2 + I^2 (X_L - X_C)^2}$$

~~$$V = \sqrt{I^2 R^2 + (X_L - X_C)^2}$$~~

~~$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$~~

~~$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$~~

2. Phaser Diagram for $X_L < X_C$

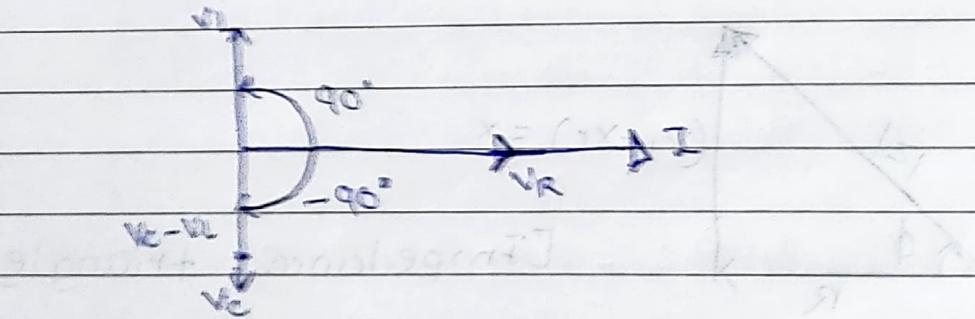


Since $X_L < X_C$ ∴ Voltage drop across Inductor is less than voltage drop across Capacitance.


$$\therefore V_L < V_C$$

$V_C > V_L$, so the resultant of V_L and V_C is $(V_C - V_L)$

Capacitive
Current

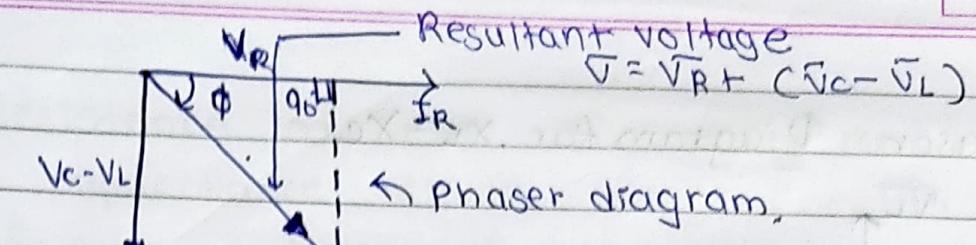

phasor diagram.

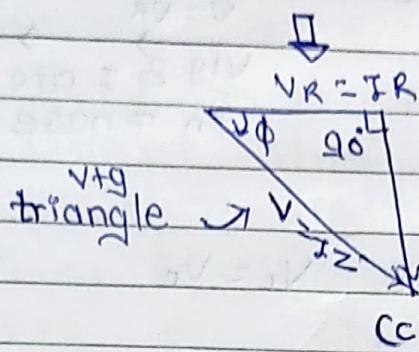

[Voltage Triangle]

From voltage triangle

$$V^2 = V_R^2 + (V_C - V_L)^2$$

$$V = \sqrt{V_R^2 + (V_C - V_L)^2}$$

Here,

$$V_R = I \cdot R, V_C = I \cdot X_C \text{ and } V_L = I \cdot X_L$$

$$V = \sqrt{I^2 R^2 + (I X_C - I X_L)^2} = \sqrt{I^2 R^2 + I^2 (X_C - X_L)^2}$$

$$V = I \sqrt{R^2 + (X_C - X_L)^2}$$


$$V = I \sqrt{R^2 + (X_C - X_L)^2}$$

$$\therefore Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\tan \phi = -\frac{(X_C - X_L)}{R} = -\frac{(V_L - V_C)}{R}$$


$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{R} \right)$$

* Impedance triangle.

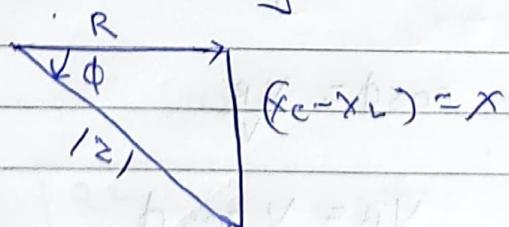


* Power triangle

$A_{RP} =$
$R P$
$A_{P} =$

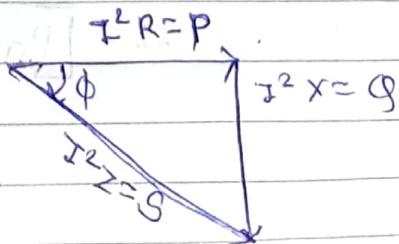

3. Phasor Diagram for $X_L = X_C$

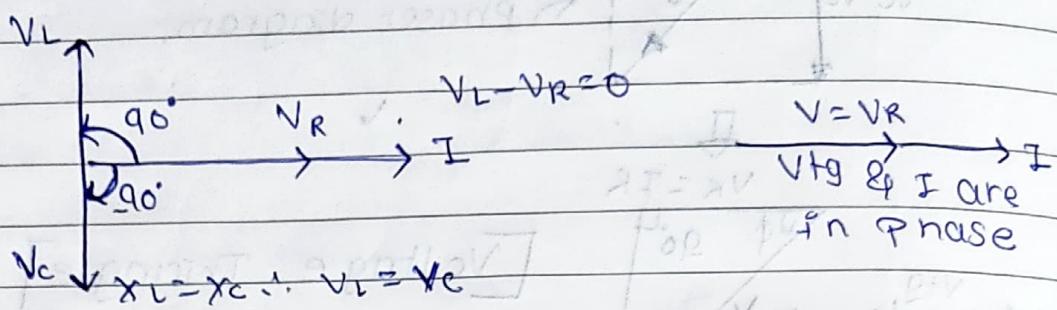

Since $X_L = X_C$ that means $V_L = V_C$

V_L & V_C will cancel each other and its resultant will be zero.

$$\therefore V_L - V_C = 0$$

* Power consumed by Series RLC circuit.

- > The average power supplied to series RLC circuit is the addⁿ of power consumed by resistor(R), inductor(L) and capacitor(C).
- > But pure inductor and capacitor do not consume any power.

$$\therefore P_{av} = I^2 R = I \cdot (I \cdot R)$$

$$\therefore [P_{av} = I \cdot V_R]$$

from v_{tg} Δ

$$\cos \phi = \frac{V_R}{V}$$

$$V_R = V \cos \phi$$

$$\therefore [P_{av} = V \cdot I \cdot \cos \phi]$$

Q A Resistance of 20Ω Inductance and of $0.05H$ and capacitance $50\mu F$ are connected in series a supply voltage of $230V, 50Hz$ is connected across this series combination. Calculate

- 1) Impedance of the circuit
- 2) Current drawn by the circuit
- 3) Phase angle b/w V_{tg} and current
- 4) Power factor of circuit
- 5) V_{tg} drop across capacitance
- 6) Active and Reactive power P, Q

Given

$$R = 20\Omega$$

$$L = 0.05H$$

$$C = 50\mu F = 50 \times 10^{-6} F$$

$$V_{rms} = 230V$$

$$f = 50Hz$$

$$\boxed{X_L = 2\pi f L}$$

$$= 2\pi \times 50 \times 0.05$$

$$\boxed{X_L = 15.707 \Omega}$$

ii)

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = 31.83 \Omega$$

$$\boxed{X_C = 31.83 \Omega}$$

As, we can see $X_C > X_L$ Hence complete circuit is capacitive in nature.

$$\boxed{i) Z = \sqrt{R^2 + (X_C - X_L)^2}}$$

$$\boxed{Z = 51.96 \Omega}$$

$$I = \frac{V}{Z} = \frac{230}{51.96}$$

$$I = 4.426 \text{ A}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$= \tan^{-1} \left(\frac{18.70 - 6.366}{20} \right)$$

$$\phi = -67.36$$

$$P.F = \cos \phi$$

$$P.F = 0.3849$$

$$V_C = I \times X_C$$

$$= 4.426 \times 6.366$$

$$[V_C = 28.1075 \text{ V}]$$

$$P = VI \cos \phi = 230 \times 4.426 \cos \phi$$

$$= 230 \times 4.426 \times 0.3849$$


$$P = 391.86 \text{ Watt}$$

$$Q = VI \sin \phi = 230 \times 4.426 \sin (-67.36)$$

$$Q = -939.53 \text{ VAR}$$

* Resonance in series R-L-C circuit
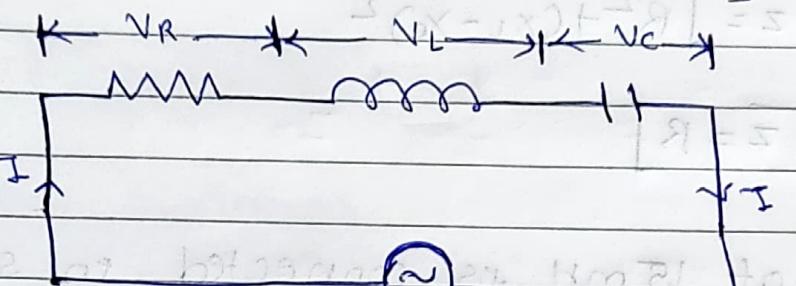
> The series resonance circuit consists of resistor (R), inductance (L) and capacitance (C) connected in series with supply voltage (V).



* Resonant frequency

Inductive reactance X_L and capacitive reactance X_C are the functⁿ of supply frequency. If the supply frequency vary both X_C & X_L varies,

At certain frequency X_L becomes equal to X_C is called series resonance & a frequency at which resonance occurs is called as resonant frequency.

- > It is denoted by f_{res}
- > Under this resonance condition current reaches the maximum value such that $I_{max} = \frac{V}{R}$ & impedance of this circuit i.e. Z falls to a minimum value. Hence $Z = R$.

As

$$X_L = X_C$$

$$2\pi f_{res} L = \frac{1}{2\pi f_{res} C}$$

$$f_{res}^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$X_L > X_C$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R$$

- (Q) A coil of 15 mH is connected in series with 25Ω Resistance and capacitor C across 230 V , 50 Hz AC supply. Find the value of this capacitor so that circuit has maximum current. Also find the power factor & power consumed of this circuit.

Q1n Given

$$L = 15 \text{ mH} = 15 \times 10^{-3} \text{ H}$$

$$R = 25 \Omega$$

$$V = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

As current reaches to a maximum value it is a resonance condition.

Under Resonance Condition

$$X_L = X_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$C = \frac{1}{(2\pi f)^2 \times L}$$

$$C = \frac{1}{4\pi^2 \times 50^2 \times 15 \times 10^{-3}}$$

$$C = 6.7847 \times 10^{-4}$$

$$Z = R$$

$$Z = 25 \Omega$$

$$\text{Power factor} = \cos\phi = 1$$

Power consumed

$$P = V I \cos\phi$$


$$I_{\max} = \frac{V}{R} = \frac{230}{25} = 9.2 A$$

$$P = 230 \times 9.2$$

$$[P = 2116 W]$$

* Basic concept of parallel AC circuits.

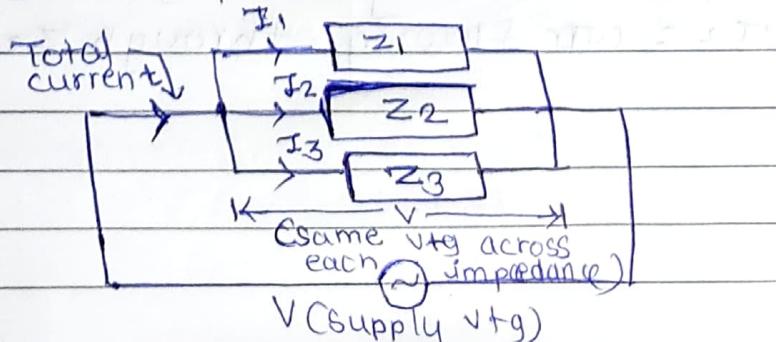- > A parallel AC circuit consists of two or more impedance connected in parallel across supply voltage 'V'.
- > Each impedance is called branch of this parallel circuit.
- > The voltage across all the impedance is same as the supply voltage 'V'.
- > According to K. But the current flowing through each impedance is different.



According to Kirchhoff's current law total current is the addition of individual current.


$$\text{i.e. } I_{\text{total}} = I_1 + I_2 + I_3$$

$$\frac{V}{Z} = \frac{V}{Z_1} + \frac{V}{Z_2} = \frac{V}{Z_{\text{eq}}} = \text{constant}$$

$$\frac{1}{Z_{\text{eq}}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

Z_{eq} is the equivalent impedance of the circuit.

* Two impedance in Parallel

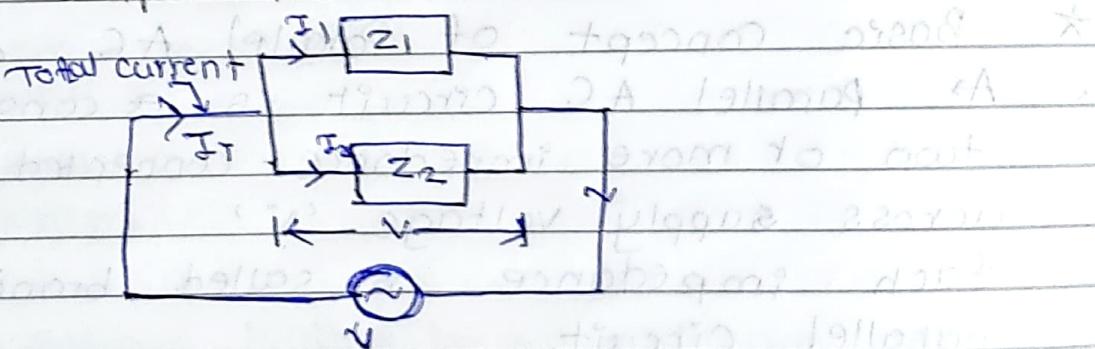

Consider two impedance Z_1 and Z_2 are connected in parallel across supply voltage V .

The different current

$$I_T = \text{Total current}$$

$$I_1 = \text{current flowing through } Z_1$$

$$I_2 = \text{current flowing through } Z_2$$

The current is given as.

$$I = \frac{V}{Z}$$

Thus I_1 & I_2 can be written as.

$$I_1 = \frac{V}{Z_1} \quad \text{and} \quad I_2 = \frac{V}{Z_2}$$

$$\text{Now } I_T = I_1 + I_2$$

$$I_T = \frac{V}{Z_T}$$

$$= \frac{V}{Z_T} = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$I_T = I_1 + I_2$$

$$I_1 = I_T \times \frac{Z_2}{Z_1 + Z_2}$$

$$I_2 = I_T \times \frac{Z_1}{Z_1 + Z_2}$$

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

- Q) Two impedance $Z_1 = 30 \angle 45^\circ \Omega$ & $Z_2 = 45 \angle 30^\circ \Omega$ are connected in parallel across 230V single phase supply calculate total impedance of this parallel circuit Find total current then power factor of this circuit, & power consumed by this circuit.

Given,

$$Z_1 = 30 \angle 45^\circ \Omega = 21.21 + j21.21$$

$$Z_2 = 45 \angle 30^\circ \Omega = 38.97 + j22.5$$

$$Z_{\text{total}} = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

$$= (30 \times 45) \angle (45 + 30)$$

$$= (21.21 + 38.97) + j(21.21 + 22.5)$$

$$= \frac{1350 \angle 75}{60.18 + j43.71}$$

$$= \frac{1350 \angle 75}{74.37 \angle 35.99}$$

$$= (1350 \div 74.37) \angle (75 - 35.99)$$

$$= 18.15 \angle 39.01$$

$$\begin{aligned} I_{\text{total}} &= \frac{V}{Z_{\text{total}}} = \frac{230 \angle 0^\circ}{18.15 \angle 39.01} \\ &= 12.67 \angle (-39.01) \end{aligned}$$

$$PF = \cos \phi$$

$$PF = \cos(-39.01)$$

$$[PF = 0.777]$$

$$P = VI \cos \phi$$

$$P = 230 \times 12.67 \times 0.777$$

$$[P =]$$

* Concept of Admittance

It is defined as the reciprocal of impedance (Z):


$$\therefore Y = \frac{1}{Z}$$

> Unit is Siemens (S) or mho(Ω^{-1})

• One Siemens

(It is admittance of network having impedance $\pm \infty$)

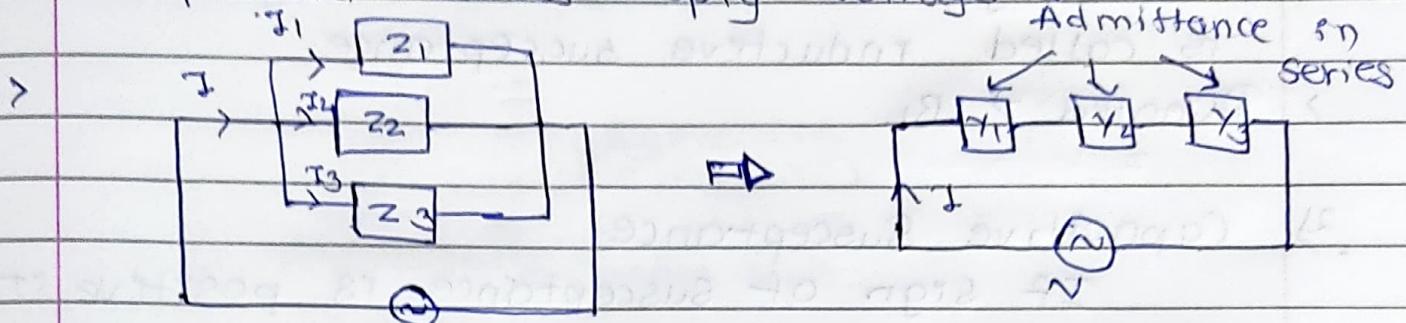- > Consider three impedances z_1, z_2, z_3 connected in parallel across supply voltage V



$$I_{\text{total}} = I_1 + I_2 + I_3$$

$$\frac{V}{z} = \frac{V}{z_1} + \frac{V}{z_2} + \frac{V}{z_3} \Rightarrow \frac{1}{z} = \frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3}$$

$$Y = Y_1 + Y_2 + Y_3 \quad \therefore Y = \frac{1}{z_{\text{parallel}}}$$

- > When impedances are connected in series parallel then admittances are in series
 > When impedances are connected in series then admittances are in parallel.

* Conductance

It is the ratio of resistance (R) to the square of impedance (z^2).

$$R = Z^2 \cdot G$$

$$\therefore G = \frac{R}{Z^2}$$

> Unit = Siemens (S) or Ω^{-1}

* Susceptance:-

It is the ratio of reactance to the square of impedance (z^2).

$$\therefore B = \frac{X}{Z^2}$$

Unit (S) or Ω^{-1} ,

Types:-

> Inductive Susceptance;

If sign of susceptance is negative, it is called inductive susceptance.

> Denoted $\rightarrow B_L$

.2) Capacitive Susceptance

If sign of susceptance is positive, it is capacitive susceptance.

> Denoted $\rightarrow B_C$

* Admittance Triangle

The equation of admittance is

$$Y = G + jB$$


↓ ↘

Real term Imaginary term

- > The conductance (G) is real part of admittance so conductance (G) is considered as reference axis.
- > Each side of triangle represents admittance conductance and susceptance.

For inductive susceptance (B_L), equation of admittance is,


Reference axis

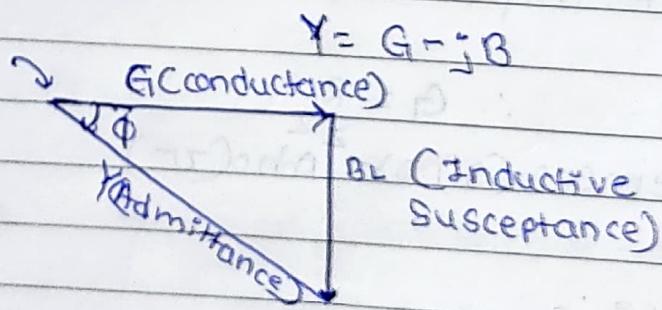

Admittance triangle of inductive susceptance

> For capacitive susceptance (Bc)

$$Y = G + jB$$

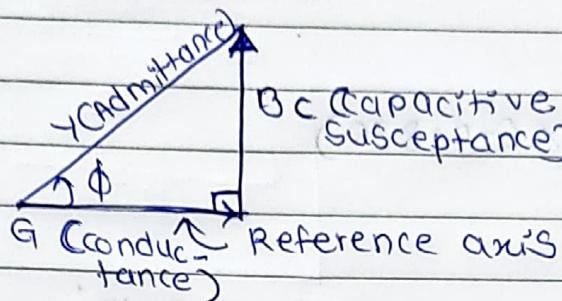

- Q) Two impedances $Z_1 = 6 + j8 \Omega$ and $Z_2 = 5 + j12 \Omega$ are connected in series across 100V 50Hz supply calculate equivalent impedance of this circuit, power factor & P, Q, S.

Q11

Given,

$$Z_1 = 6 + j8 \Omega$$

$$Z_2 = 5 + j12 \Omega$$

$$Z_{eq} = Z_1 + Z_2$$

$$Z_{eq} = 11 + j20 \Omega = 22.82 \angle 61^\circ 18'$$

$$PF = \cos \phi$$

$$= \cos 61^\circ 18'$$

$$[PF = 0.48]$$

$$I = \frac{V}{Z} = \frac{100 \angle 0}{22.82 \angle 61^\circ 18}$$

$$I = 4.38 \angle -61^\circ 18$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

$$S = VI$$

$$P = 100 \times 4.38 \times 0.48$$

$$P = 210.24$$

$$\Phi = VI \sin \phi$$

$$= 100 \times 4.38 \times (-0.876)$$

$$= -383.68$$

$$S = 438$$

lags V by $61^\circ 18'$

$$V = 100$$

$$I = 40.881$$

$$-2.9742 = 7.5$$

$$-2.2748 = 5.8$$

$$5.8715 = 0.0000$$

$$314.24 - 58.68 = 256.55411 = P$$

$$h_{20} = 77$$

$$214.24 - 32 =$$

$$182.0 = 77$$

$$214.24 - 58.68 = V = 5$$

$$214.24 - 58.68 = 77$$

$$\Phi_{ent} = 9$$

$$\Phi_{ext} = 0$$