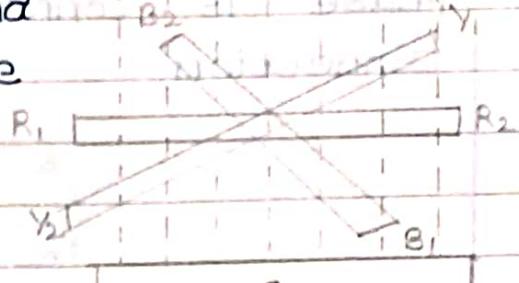


## Poly Phase Ac circuit.

Page No.:	
-----------	--

The Symetric circuit the all are separated by same angel and induced emf same magnitude and same frequency.




$$\bar{e} = \bar{e}_R + \bar{e}_Y + \bar{e}_B \\ = E_m \sin \omega t + E_m \sin(\omega t - 120^\circ) \\ + E_m \sin(\omega t + 120^\circ)$$

$$= E_m \sin \omega t + E_m [\sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ] \\ + E_m [\sin \omega t \cos 120^\circ + \cos \omega t \sin 120^\circ]$$


$$= E_m \sin \omega t + 2E_m \sin \omega t \left(-\frac{1}{2}\right) \\ \therefore \bar{e} \Rightarrow 0 \\ \therefore \bar{e}_R + \bar{e}_Y + \bar{e}_B = 0$$

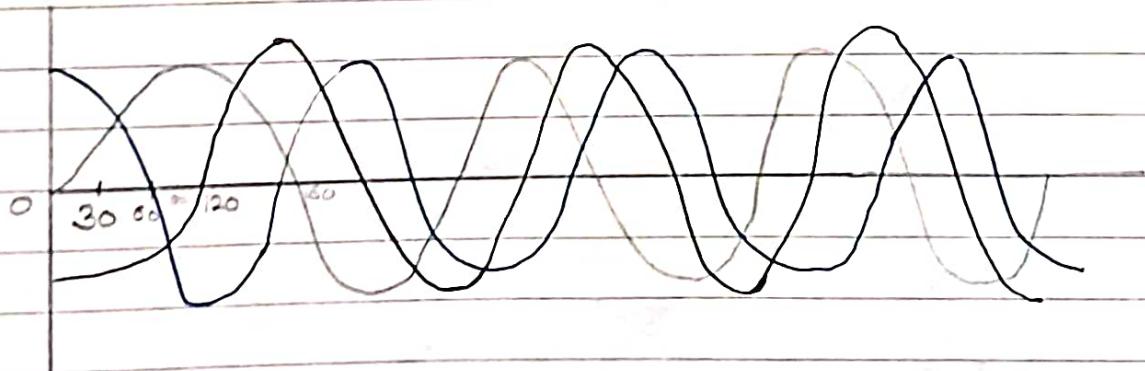$e_R = E_m \sin \omega t$   
 $e_Y = E_m \sin(\omega t - 120^\circ)$   
 $e_B = E_m \sin(\omega t + 120^\circ)$   
 $= E_m \sin(\omega t + 120^\circ)$


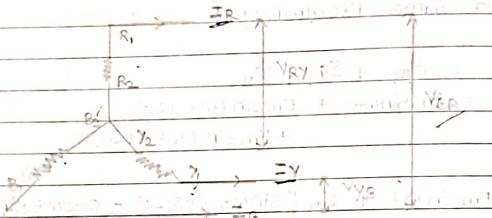
### \* Star connection (Y)

when second terminal of each of the phase is connected together it form star connection.




Line current : current flowing through line

$$I_R = I_Y = I_B = I_T$$

Line Voltage = Voltage from line to line

$$V_{RY} = V_{BY} = V_{CY}$$

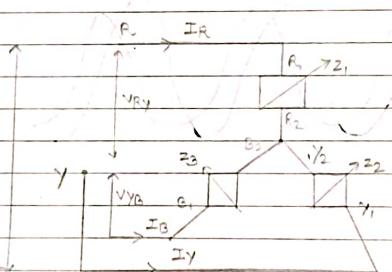

Balance load : Angle and magnitude of each impedance must be same.

Phase Voltage : Voltage from phase to phase.

$$V_{RN} = V_{YN} = V_{BN} = V_{ph}$$

Phase current : current flowing through phase

$$I_R = I_Y = I_B = I_{ph}$$


$$I_L = I_{ph}$$

$$\bar{V}_{RY} = \bar{V}_{RN} + \bar{V}_{NY} = \bar{V}_{RN} - \bar{V}_{YN}$$

$$\bar{V}_{BY} = \bar{V}_{YN} + \bar{V}_{NB} = \bar{V}_{YN} - \bar{V}_{BN}$$

$$\bar{V}_{CY} = \bar{V}_{BN} + \bar{V}_{NR} = \bar{V}_{BN} - \bar{V}_{RN}$$

Reference as phase voltage \*\*

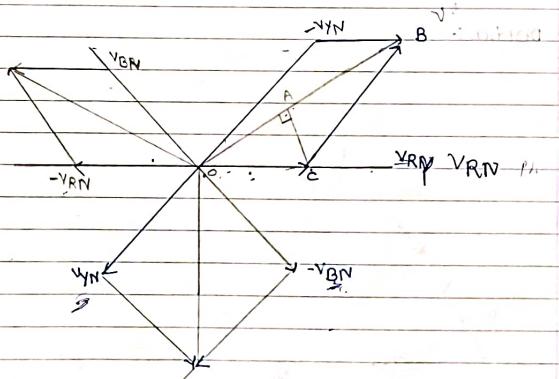

In  $\triangle OAC$

$$OA = \frac{1}{2} OB$$

$$OC = V_{ph}$$

$$OA = \frac{1}{2} VL$$

$$\angle AOK = 30^\circ$$

$$\cos 30^\circ = \frac{OA}{OC} \Rightarrow \frac{\sqrt{3}}{2} = \frac{V_L}{2V_{ph}}$$

$$V_L = \sqrt{3} V_{ph} \quad \text{* 4}$$

power,  $P = V_{ph} I_{ph} \cos \phi$ .

$$= 3 \times \frac{V_L}{\sqrt{3}} I_L \cos \phi. \quad \dots \text{3 Phase.}$$


$$P = \sqrt{3} \cdot V_L I_L \cos \phi.$$

$$Q = \sqrt{3} \cdot V_L I_L \sin \phi.$$

$$S = \sqrt{3} V_L I_L$$


$$P = \sqrt{3} V_L I_L \cos \phi.$$

\* Delta:

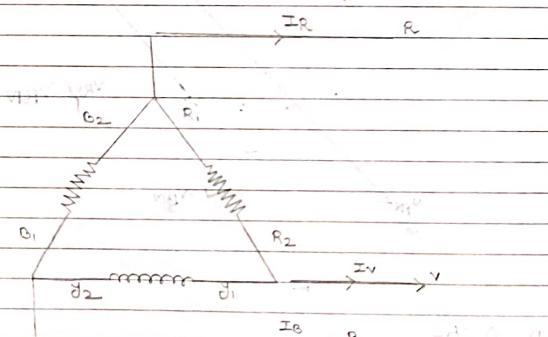

$$I_R = I_Y = I_B = I_L$$
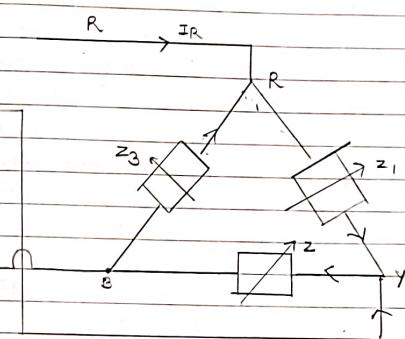
$$V_{RY} = V_{YB} = V_{BR} = V_L \text{ II.}$$



$$V_{RY} = V_{YB} = V_{BR} = V_{ph}$$

$$I_{RY} = I_{YB} = I_{BR} = I_{ph}$$

$$V_L = V_{ph} \quad \text{* 4}$$

at node R,

KCL

$$\bar{I}_R + \bar{I}_{BR} = \bar{I}_{RY}$$

$$\bar{I}_R = \bar{I}_{RY} - \bar{I}_{BR} \quad \text{--- ①}$$

at node Y

KCL


$$\bar{I}_Y + \bar{I}_{RY} = \bar{I}_{YB}$$

$$\bar{I}_Y = \bar{I}_{YB} - \bar{I}_{RY} \quad \text{--- ②}$$

at node B. KCL

$$\bar{I}_Z + \bar{I}_{YB} = \bar{I}_{BR}$$
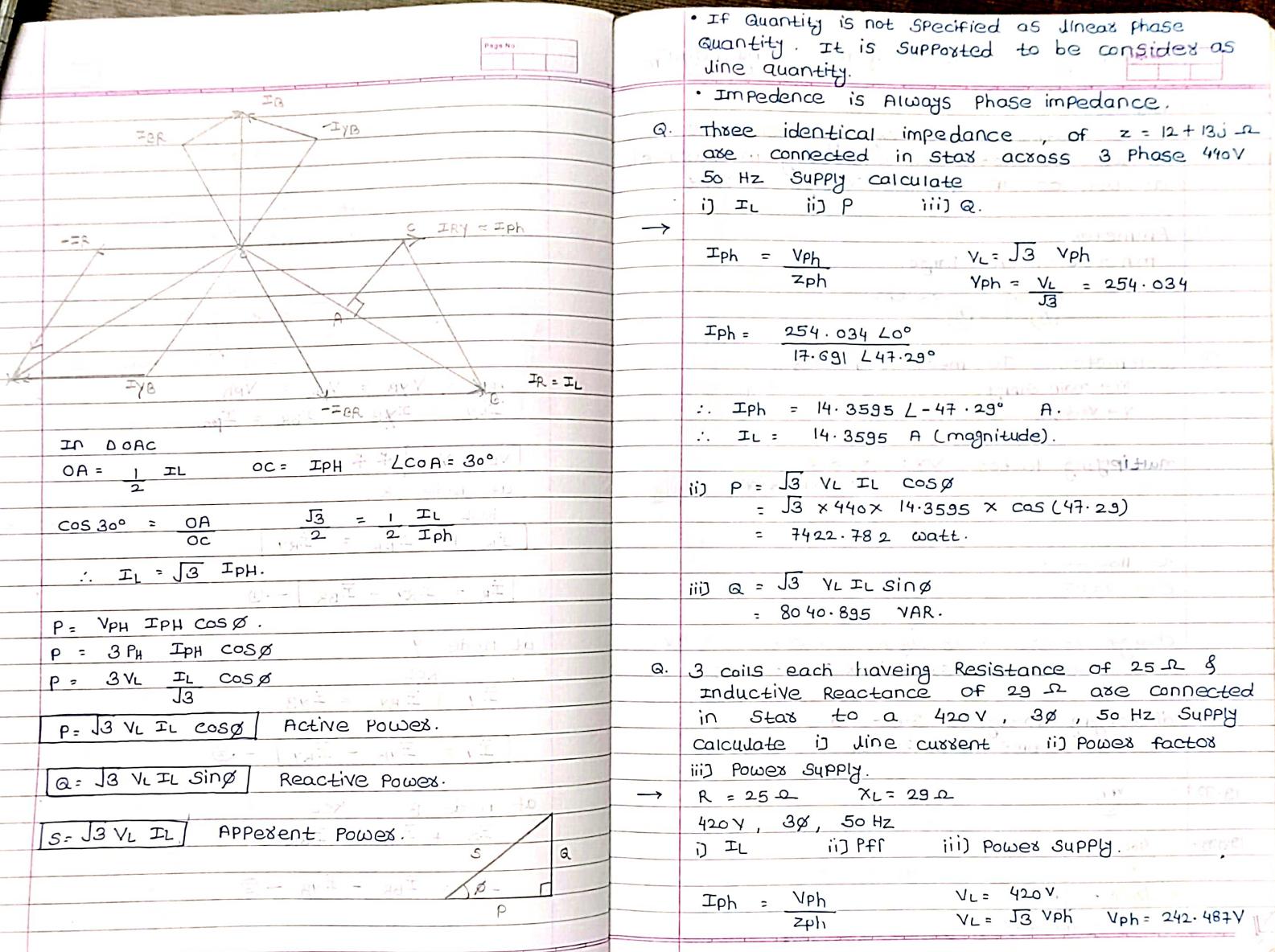
$$\bar{I}_Z = \bar{I}_{BR} - \bar{I}_{YB} \quad \text{--- ③}$$



## Safety Precautions & measuring equipm.

1) Voltmeter: Voltmeter has very high resistance so we use voltmeter connecting in parallel as well as in parallel voltage is const.

2) Ammeter: mA  $\rightarrow$  0  $\rightarrow$  100 A. Range  
 $\rightarrow$  0-10 (A)  $\rightarrow$  0-5 (A)

3) Wattmeter: To measure power

$m \rightarrow$  main supply

$v \rightarrow$  voltage

Multiplying factor:  $V \times I \times \cos \phi$

Full scale deflection

$$R = 1100 \Omega$$

$$C = 22 \mu F$$

$$\text{charging voltage} \rightarrow 18 \text{ sub divisions} \times 0.2 = 3.6 \text{ V}$$

$$\text{time} \rightarrow 4 \text{ sub divisions} \times 5 = 20 \text{ ms}$$

$$\text{discharging voltage} \rightarrow 3.6 \rightarrow 0$$

$$\text{time} \rightarrow 20 \text{ ms}$$

$$19.999 = \frac{V_{ph}}{Z}$$

$$19.999 = \frac{400}{Z}$$

$$Z = \sqrt{R^2 + X^2}$$

$$400 = \sqrt{R^2 + X^2}$$

$$Z_{ph} = R + j(X_L - X_C) \quad \therefore X_C = 0$$

$$Z_{ph} = 25 + j29 \Omega$$

$$= 38.288 \angle 49.236^\circ$$

$$I_{ph} = \frac{242.487}{38.288} \angle 49.236^\circ$$

$$I_{ph} = 6.333 \angle 49.236^\circ$$

$$I_L = 6.333 \text{ A (magnitude)}$$

$$i) Pf = \cos \phi = 0.652 = \cos(49.236^\circ)$$

$$ii) P = \sqrt{3} V_L I_L \times \cos \phi$$

$$= \sqrt{3} \times 420 \times 6.333 \times 0.653$$

$$= 2659.86 \text{ watt.}$$

$$iii) Q = 3006.954 \text{ watt.}$$

Q. A delta connected balanced load across 400V, 3Ø consists of 3 identical impedances each equal to  $17 + 9j \Omega$ . Find  $I_L$ , Reactive power, Active power.

$$\rightarrow V_L = 400 \text{ V}, 3\phi, 50 \text{ Hz} \quad (\Delta \text{ delta})$$

$$Z_{ph} = 17 + 9j \Omega$$

$$V_L = V_{ph}$$

For  $\Delta$ .

$$I_L = \sqrt{3} I_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400 \angle 0^\circ}{17 + 9j} = \frac{400}{19.235} \angle 27.897^\circ$$

$$I_{ph} = 20.795 \angle 27.897^\circ$$

$$I_L = \sqrt{3} \times 20.795$$

$$= 36.018 \text{ A.}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 36.018 \times \cos(27.897)$$


$$= 22054.101 \text{ watt.}$$

$$Q = \sqrt{3} V_L I_L \sin \phi = 11675.566 \text{ VAR.}$$

## single phase transformer.

Transformer is used to transform electricity from one ckt to another by increase or decrease voltage but with same frequency or without changing frequency.

### working principle of transformer.

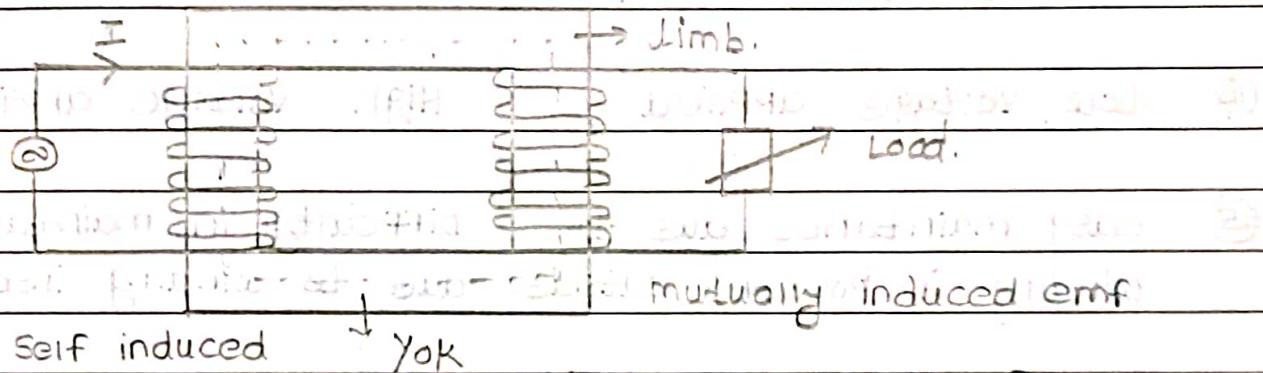


when AC supply is given to first coil then current starts flowing through ckt. due to flow current flux will produce. due to AC supply there is change in flux so Accn to faraday's law whenever change in flux linkage there will be induced emf so in coil one is self induced emf. At secondary side if there is no load so no current but due to current in first coil emf gets induced in second coil ∴ in second coil there is mutually induced emf.

core is either of I or L shape.

material is high grade stainless steel laminated core.

core type	Shell Type
① winding is present around core	core is present around winding.
② 2 limbs	3 limbs.
③ 1 Path for flow $\phi$ .	2 Path for flow of flux.
④ Low voltage applied	High Voltage applied.
⑤ easy maintenance due to winding is present outside.	difficulty in maintenance due to winding inside a core
⑥ Natural cooling.	no natural cooling, cooling material is required for cooling.

\* Ratios of  $X_{max}$ :

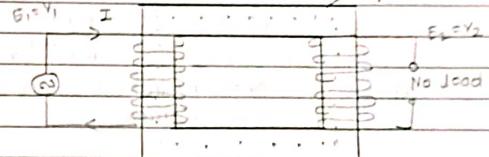

$$E_1 = 4.44 \times \Phi_m \times f \times N_1$$

$$E_2 = 4.44 \times \Phi_m \times f \times N_2$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K \quad \text{... Transformation Ratio}$$

If  $K > 1$ ,  $N_2 > N_1$ ,  $E_2 > E_1$ , Stepup Transformer.

If  $K < 1$ ,  $N_2 < N_1$ ,  $E_2 < E_1$ , Stepdown.

If  $K = 1$ ,  $N_2 = N_1$ ,  $E_2 = E_1$ , one: one

\* Voltage ratio:

$$\frac{E_2}{E_1} = \frac{V_2}{V_1} = K = \frac{N_2}{N_1}$$

\* Current ratio:

For ideal transformer:

$$V_{pp} = O/P.P$$

$$V_1 I_1 = V_2 I_2$$

$$\frac{I_1}{I_2} = \frac{V_2}{V_1}$$

$$\frac{N_2}{N_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2} = K$$

$\frac{I_1}{I_2} \rightarrow$  current ratio.

LOSSES IN  $\times_{\text{max}}$ :

CORE LOSS ( $P_c$ ) :- constant losses.

i) Hysteresis loss :  $K_h B_m^{1.67} f v$

whereas  $K_h \rightarrow$  hysteresis constant  
 $v \rightarrow$  volume

ii) Eddy current loss :  $K_e B_m^2 f^2 t^2$   
 $K_e \rightarrow$  Eddy current const  
 $t \rightarrow$  thickness of core

COPPER LOSS ( $P_{cu}$ ) :- variable losses due to current.

$$P_{cu} = I_1^2 R_1 + I_2^2 R_2$$

$$= I_1^2 (R_1 + R_2)$$

$$P_{cu} = I_1^2 R_{1e} \text{ OR } I_2^2 R_{2e}$$

$$R_{1e} = R_1 + R_2$$

$$R_{1e} = \frac{R_1 + R_2}{K^2} \quad \dots \text{equivalent resist. w.r.t. to primary.}$$

↑ transformation or form

$$R_{2e} = R_1' + R_2 \quad \dots \text{equi resist. w.r.t. to secondary}$$

$$R_{2e} = K^2 R_1 + R_2$$

$$(P_{cu})_{FL} = (I^2)_{FL} \cdot R$$

50%  $I_1$   $I_2 = 0.5$

$$(P_{cu})_{FL} = \frac{(I^2)_{FL}}{4} \times R$$

$$(P_{cu})_{FL} = (I^2)_{FL}^2 \times R \times 4$$

$$(P_{cu})_{HL} = (I^2)_{FL}^2 \times R$$

$$(P_{cu})_{FL} = 4$$

$$(P_{cu})_{HL}$$

$$\therefore (P_{cu})_{HL} = \frac{1}{4} \times (P_{cu})_{FL}$$

$$\therefore (P_{cu})_{HL} = n^2 \times (P_{cu})_{FL}$$

\* KVA Rating of  $\times_{\text{max}}$ :

$$(V_1 \cdot I_1) = (\text{VA rating})_1$$

$$(V_2 \cdot I_2) = (\text{VA rating})_2$$

$$(\text{KVA rating}) = \frac{V_1 I_1}{1000}$$

$$(\text{KVA rating}) = \frac{V_2 I_2}{1000}$$

$$(I_1)_{FL} = (\text{KVA rating}) \times 1000$$

$$(I_2)_{FL} = (\text{KVA rating}) \times 1000$$

\* Efficiency of  $\times_{\text{max}}$ :

$$\% \eta = \frac{\text{O/P P}}{\text{I/P P}} \times 100$$

O/P P  $\leq$  I/P P ... Always.

$$\frac{I}{P} = \frac{O/P P}{P} + \text{josses}$$

$$\frac{I}{P} = \frac{O/P P}{P} + P_i + (P_{cu})_{FL}$$

$$\eta = \frac{O/P P}{O/P P + P_i + (P_{cu})_{FL}}$$

$$\therefore \eta = \frac{V_2 I_2 \cos\phi}{V_2 I_2 \cos\phi + P_i + (P_{cu})_{FL}}$$

$\eta$  at 50% loaded  $n = 0.5$

$$(\eta)_{n=0.5} = \frac{n V_2 I_2 \cos\phi}{n V_2 I_2 \cos\phi + P_i + n^2 (P_{cu})_{FL}}$$

Q. A 70 KVA, 1200/600 V, single phase, 50 Hz,  $X_{mex}$  has iron loss of 750 W & full load copper loss of 1300 W. Find  $\eta$  % at full load with power factor 0.8 lagging  $\rightarrow$  no effect.

ii) find efficiency at HL pf = 1.

$$\eta = \frac{(VA \text{ rating}) \times \cos\phi}{(VA \text{ rating}) \cos\phi + P_i + (P_{cu})_{FL}} \times 100$$

$$= \frac{70 \times 1000 \times 0.8}{70 \times 1000 \times 0.8 + 750 + 1300} \times 100$$

$$= 96.46 \%$$

$$ii) \eta = \frac{0.5 \times 70 \times 1000}{0.5 \times 70 \times 1000 + 750 + 0.25 \times 1300} \times 100$$

$$\eta = 97.02 \%$$

A. Primary Voltage  
Secondary  
has FL copper loss of 1700 W. & iron loss of 800 watt. Find  $X_{mex}$  eff. at i) FL with  $\cos\phi = 0.7$  leading  
ii) A HL with  $\cos\phi = 0.5$  lagging

$$i) \eta = \frac{65 \times 1000 \times 0.7}{65 \times 1000 \times 0.7 + 800 + 1700} \times 100$$

$$= 94.79 \%$$

$$ii) \eta = \frac{0.5 \times 65 \times 1000 \times 0.5}{0.5 \times 65 \times 1000 \times 0.5 + 800 + 0.25 \times 1700} \times 100$$

$$= 92.98 \%$$

\* condition for maximum efficiency:

$$\frac{d\eta}{dI_2} = 0$$

$$\frac{d}{dI_2} \left[ \frac{V_2 I_2 \cos\phi}{V_2 I_2 \cos\phi + P_i + I_2^2 R_{2e}} \right]$$

$$\frac{d}{dI_2} \left[ \frac{V_2 I_2 \cos\phi}{V_2 I_2 \cos\phi + P_i + I_2^2 R_{2e}} \right] = 0$$

$$\left[ V_2 I_2 \cos\phi + P_i + I_2^2 R_{2e} \right] V_2 \cos\phi - \left[ V_2 I_2 \cos\phi \right] \times \left[ V_2 \cos\phi + 2 I_2 R_{2e} \right] = 0$$

$$\left[ V_2 I_2 \cos\phi + P_i + I_2^2 R_{2e} \right] V_2 \cos\phi - \left[ V_2 I_2 \cos\phi \right] \times \left[ V_2 \cos\phi + 2 I_2 R_{2e} \right] = 0$$

$$[V_2 I_2 \cos\phi + P_i + I_2^2 R_{2e}] = V_2 I_2 \cos\phi + 2 I_2^2 R_{2e}$$

$$P_i = 2 I_2^2 R_{2e} - I_2^2 R_{2e}$$

$$\therefore P_i = I_2^2 R_{2e}$$

∴  $P_i = P_{cu}$  \* condition for maximum efficiency.

IMP Note:-

Copper losses should be equal to iron losses.

not iron losses equal to copper losses  
bcz iron losses are constant they are not changing & copper losses are variable

\* Load current at  $\eta_{max}$ .

$$P_{cu} = P_i$$

$$I_2^2 R_{2e} = P_i$$

but,

$$I_2 = I_{2m}$$

$$I_{2m}^2 R_{2e} = P_i$$

$$I_{2m} = \sqrt{\frac{P_i}{R_{2e}}}$$

divide by  $(I_2)_{FL}$ .

$$\frac{I_{2m}}{(I_2)_{FL}} = \sqrt{\frac{P_i}{R_{2e}}}$$

$$I_{2m} = \sqrt{\frac{P_i}{(I_2)_{FL} R_{2e}}}$$

$$\therefore I_{2m} = (I_2)_{FL} \sqrt{\frac{P_i}{(P_{cu})_{FL}}}$$

\* KVA Rating at  $\eta_{max}$ :

$$(KVA \text{ Rating}) = \frac{V_2 I_2}{1000}$$

$$(KVA \text{ Rating})_{\eta_{max}} = \frac{V_2 I_{2m}}{1000}$$

$$(KVA \text{ Rating})_{\eta_{max}} = \frac{V_2 (I_2)_{FL}}{1000} \times \sqrt{\frac{P_i}{(P_{cu})_{FL}}}$$

$$\therefore (KVA \text{ Rating})_{\eta_{max}} = (KVA \text{ Rating})_{FL} \times \sqrt{\frac{P_i}{(P_{cu})_{FL}}}$$

$$\therefore \eta_{max} = (\eta_{max})_{FL} \times \frac{(\eta_{max})_{FL} \times \cos\phi \times 100}{(\eta_{max})_{FL} \times \cos\phi + 2P_i}$$

Q. A  $\times$ me is rated at 1200 KVA at FL its copper loss is 1500 watt & its iron loss is 750 watt. Find  $\eta$  at FL for power factor 0.8 lagging.

i)  $\eta$  at HL for power factor unity.  
ii)  $\eta$  at 75% load with power factor 0.9 lagging.

iii) Load kVA for max efficiency.  
iv) max efficiency at power factor  $(0.75)_{load}$

→ i)  $n = \frac{(VA \text{ Rating}) \times \cos\phi}{(VA \text{ Rating}) \times \cos\phi + P_i + (P_{cu})_{FL}}$

$$= \frac{120 \times 1000 \times 0.8}{120 \times 1000 \times 0.8 + 760 + 1500} \times 100$$

$$= 97.69 \%$$

ii)  $n = \frac{n(VA \text{ Rating}) \times \cos\phi}{n(VA \text{ Rating}) \times \cos\phi + P_i + n^2(P_{cu})_{FL}} \times 100$

$$\eta_{HL} = \frac{0.5 \times 120 \times 1000 \times 1}{0.5 \times 120 \times 1000 + 760 + 0.25 \times 1500} \times 100$$

$$= 98.14 \%$$

iii)  $\eta_{75\%} \therefore n = 0.75$

$$\eta_{75\%} = \frac{0.75 \times 120 \times 1000 \times 0.9}{0.75 \times 120 \times 1000 \times 0.9 + 760 + 0.5625 \times 1500} \times 100$$

$$= 98.058 \%$$

iv)  $(KVA)_{n\max} = 120 \times \frac{760}{1500}$

$$= 85.4166$$

v) consider this max KVA for  $n_{\max}$ .

$$\eta_{\max} = \frac{85.4166 \times 1000 \times 0.75}{85.4166 \times 1000 \times 0.75 + 2 \times 760} \times 100$$

$$= 97.682 \%$$

Q. A 300 kVA Single phase transformer has iron loss of 1.8 kwatt. Full load copper loss 2000 watt. Calculate  $(n)_{FL}$  for  $\cos\phi = 0.8$  lag &  $(n)_{\max}$  at  $0.8 = \cos\phi$  lag.

$$(n)_{FL} = \frac{V \times 300 \times 1000 \times 0.8}{300 \times 1000 \times 0.8 + 1.8 \times 1000 + 2000} \times 100$$

$$= 98.44 \%$$

$(n)_{\max} :$

$$(KVA)_{\max} = \frac{300 \times 1.8 \times 1000}{2000} = 284.604$$

$$\eta_{\max} = \frac{284.604 \times 1000 \times 0.8}{284.604 \times 1000 \times 0.8 + 2 \times 1.8 \times 1000} \times 100$$

$$= 98.44 \%$$

\* Voltage Regulation :-

$$\% \text{ Regn} = \frac{V_{no \text{ load}} - V_{FL}}{V_{FL}} \times 100 \quad \text{per unit}$$

\* Regn w.r.t. Sec

\* Regn =  $\frac{V_{no \text{ load}} - V_{FL}}{V_{NL}} \times 100 \quad \text{Total Regulation}$

% regn w.r.t Secondary

$$\% \text{ regn} = \frac{I_2 R_{2e} \cos \phi + I_2 X_{2e} \sin \phi}{V_2} \times 100 \rightarrow \text{lagging}$$

, -> lead

% regn w.r.t primary

$$\% \text{ regn} = \frac{I_1 R_{1e} \cos \phi + I_1 X_{1e} \sin \phi}{V_1} \times 100$$

$$R_{2e} = R_2 + R_1' = R_2 + R_1 k^2$$

$$R_{1e} = R_1 + R_2' = R_1 + \frac{R_2}{k^2}$$

$$X_{2e} = X_2 + X_1' = X_2 + X_1 k^2$$

$$X_{1e} = X_1 + X_2' = X_1 + \frac{X_2}{k^2}$$

- Q. A 200 KVA 1Ø transformer has primary Voltage 2500 Volt. & sec. Voltage 400 V. the Supply frequency is 50 Hz. the total effective Resistance & Reactance w.r.t primary are 0.5 ohm & 2 ohm respectively calculate voltage regn xmes with 0.8 power factor lagging.

ii) Find % regn with unity P.F.

Given.

$$V_1 = 2500$$

$$V_2 = 400$$

$$200 \text{ KVA}$$

$$f = 50 \text{ Hz}$$

$$R_{1e} = 0.5 \text{ ohm}$$

$$X_{1e} = 2 \text{ ohm}$$

$$ij) P.F = (0.8) \text{ lag.}$$

$$\% \text{ regn} = \frac{I_1 R_{1e} \cos \phi + I_1 X_{1e} \sin \phi}{V_1} \times 100$$

$$(I_1)_{FL} = \frac{(\text{KVA Rating}) \times 1000}{V_1} \quad \cos \phi = 0.8$$

$$= \frac{200 \times 1000}{2500} = 80 \quad \phi = 36.86^\circ$$

$$\sin \phi = 0.6$$

$$\% \text{ regn} = \frac{(80 \times 0.5 \times 0.8) + (80 \times 2 \times 0.6)}{2500} \times 100$$


$$= 5.12 \%$$

iii) when PF unity then  $\sin \phi = 0$ .

$$\% \text{ regn} = \frac{80 \times 0.5 \times 1}{2500} \times 100$$

$$= 1.6 \%$$

\* Direct loading test :-

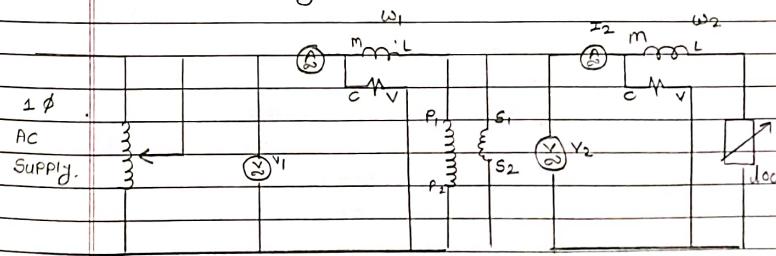

$$N_1 > N_2$$


so step down,  $X_{mes}$

$$\% \eta = \frac{\omega_2}{\omega_1} \times 100$$

no load voltage.

$$\% \text{ regn} = \frac{E_2 - V_2}{E_2} \times 100$$

IMP graph draw exam.

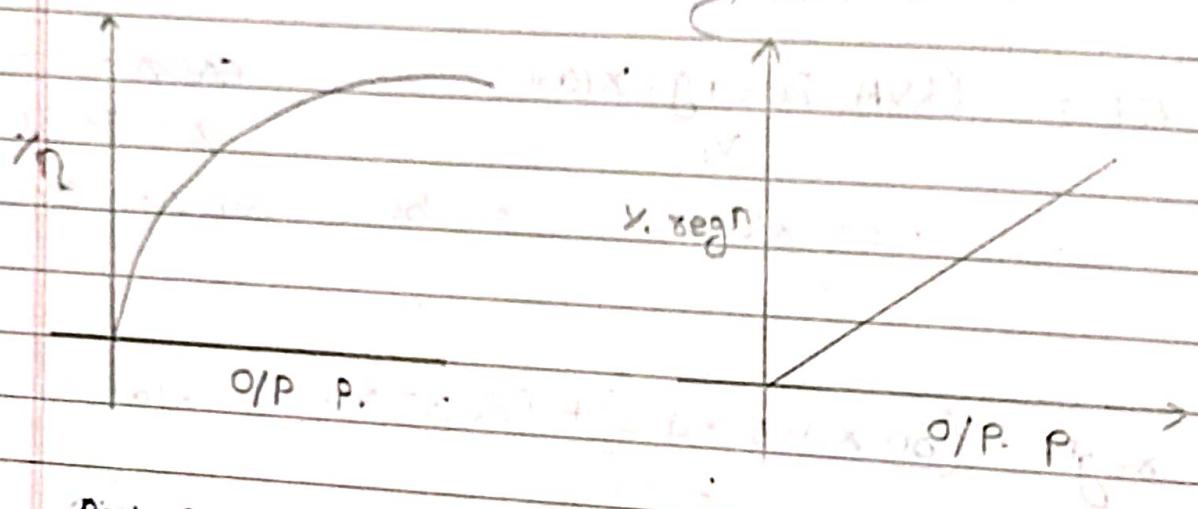

$\frac{d}{dx}$  Auto Xmax.

at max output efficiency point

total load power

load

load

Max efficiency point